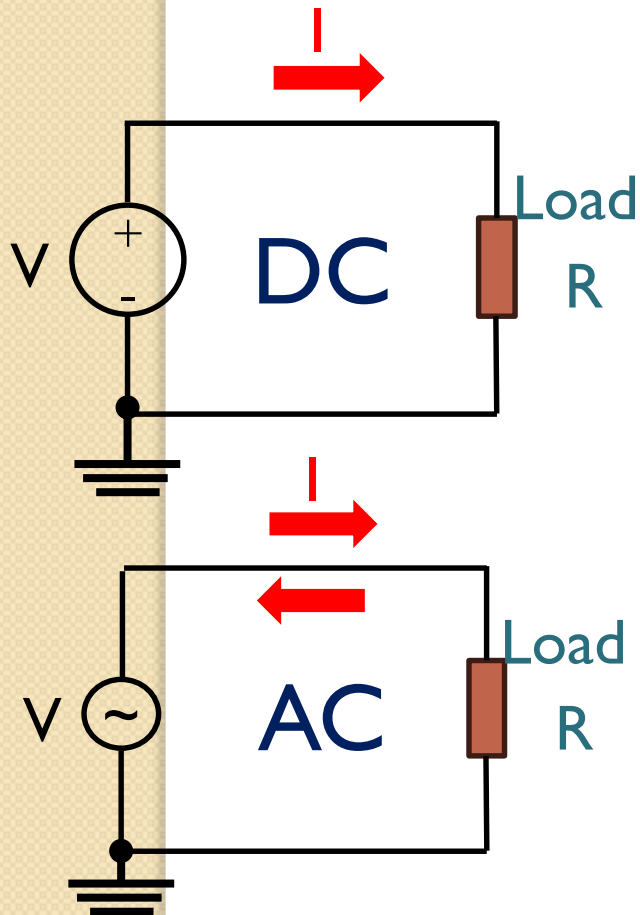


Tutorial 2: DC Regulation & Pulse Generation

Power Sources and Regulation




DC power supply



Signal generator

Draw waveforms here

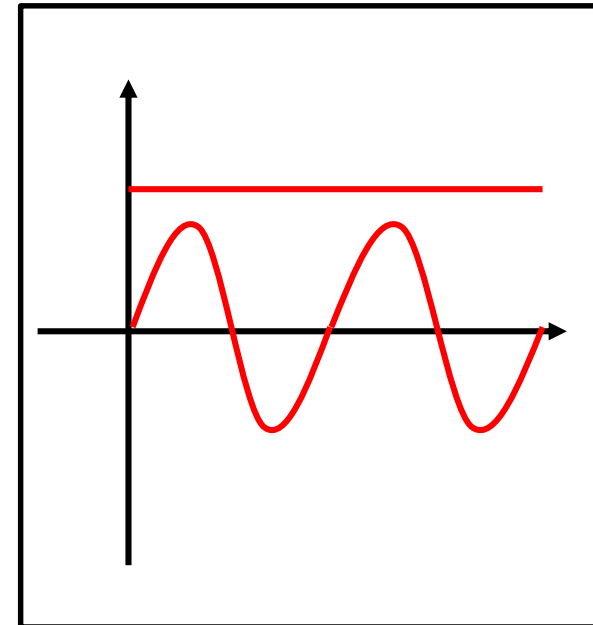


DC to DC Conversion

- When do you need DC to DC?
 - Eg. Your phone needs 9V to operate, but the motion sensor only needs 5V; you **don't want to insert two batteries!**
- Version I: Zener Diode



Zener Diode $V_{bd} \approx -5.7V$

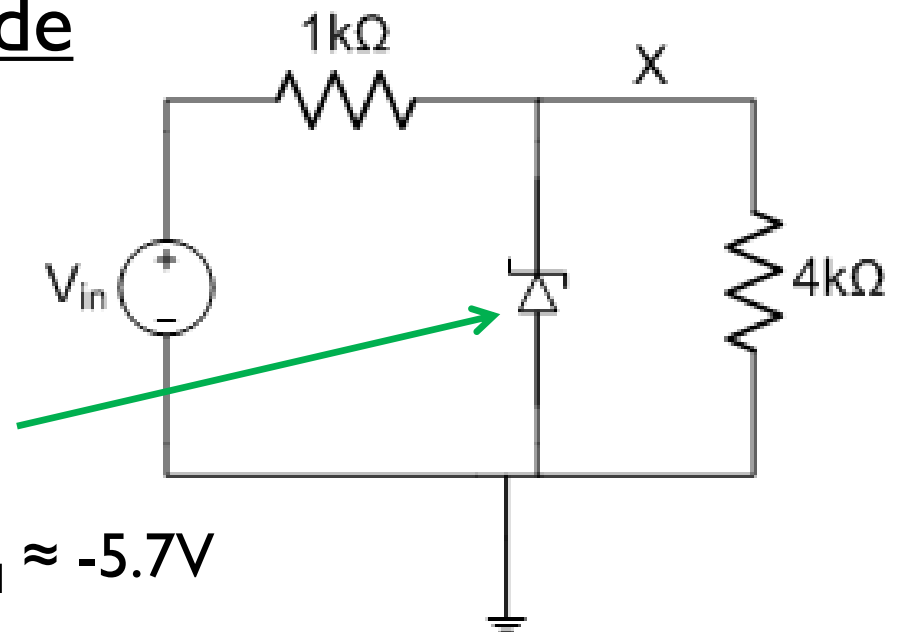


DC to DC Conversion

- Version II: Voltage Regulator

Voltage Regulator LM7805

12V Power Supply

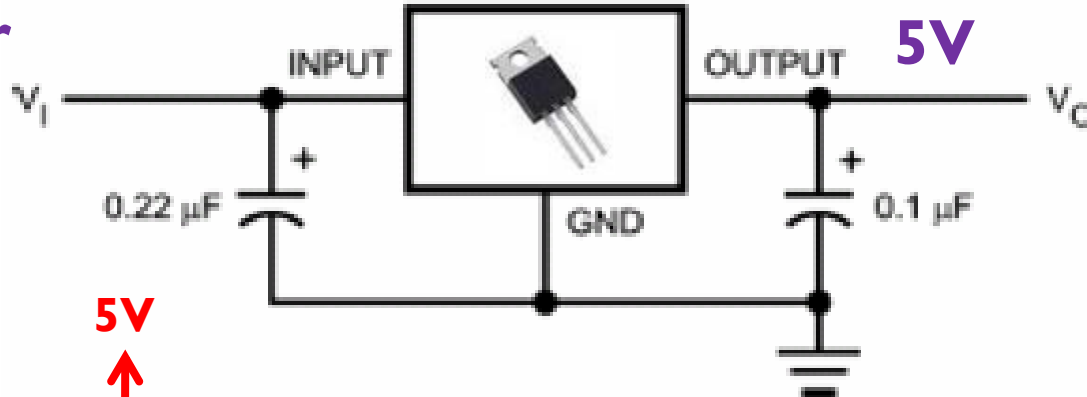

Ground

0V


5V

0.1 μ F

0.22 μ F




12V

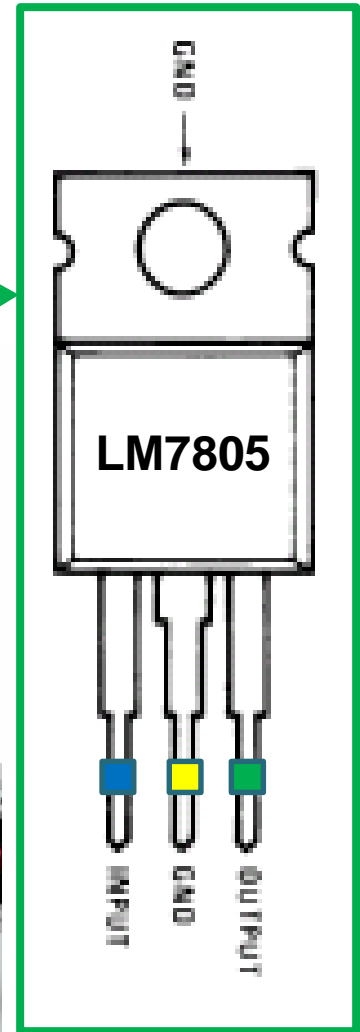



Let's learn about pulse

- A rectangular pulse looks like this.

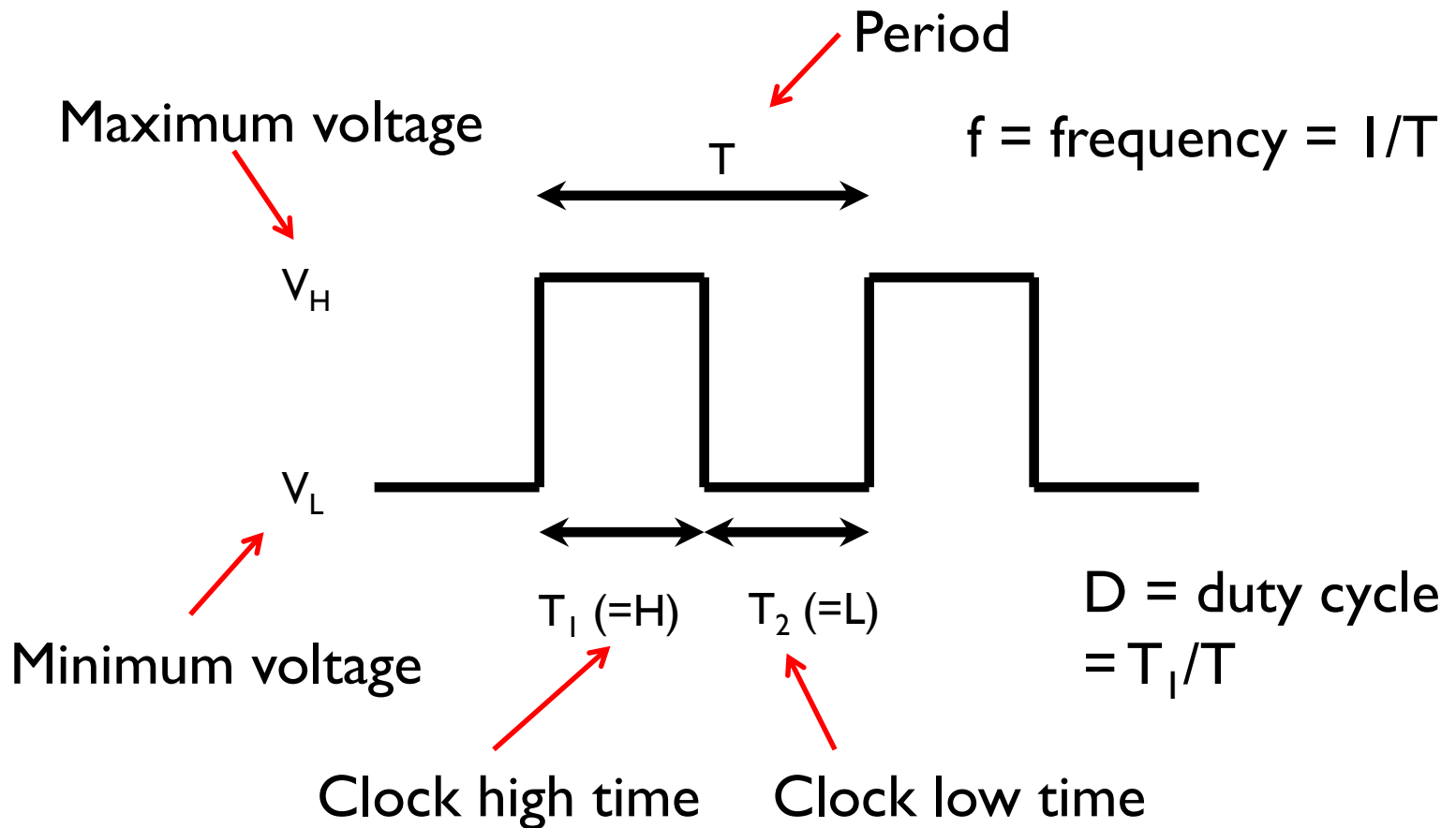

Now let's build the actual circuit

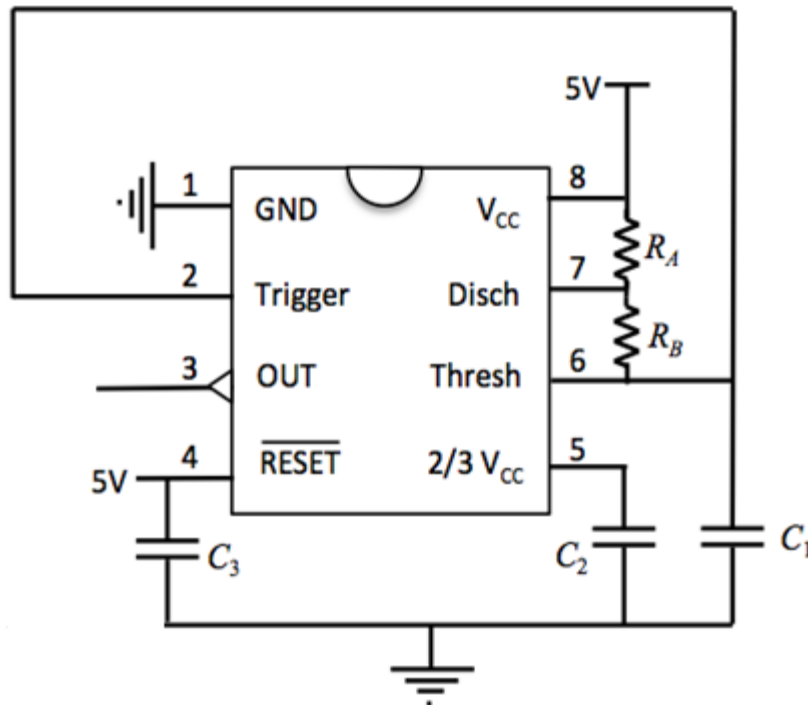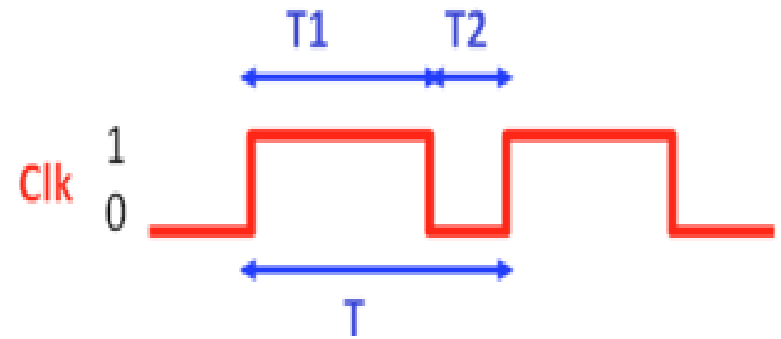- This is a NE555 timer. Equations given.



$$T1 = 0.7 (R_A + R_B) C_1$$


$$T2 = 0.7 (R_B) C_1$$

$$T = 0.7 (R_A + 2R_B) C_1$$

Observation:

Duty Cycle \geq **50%**

Lab#02: Experiment 3

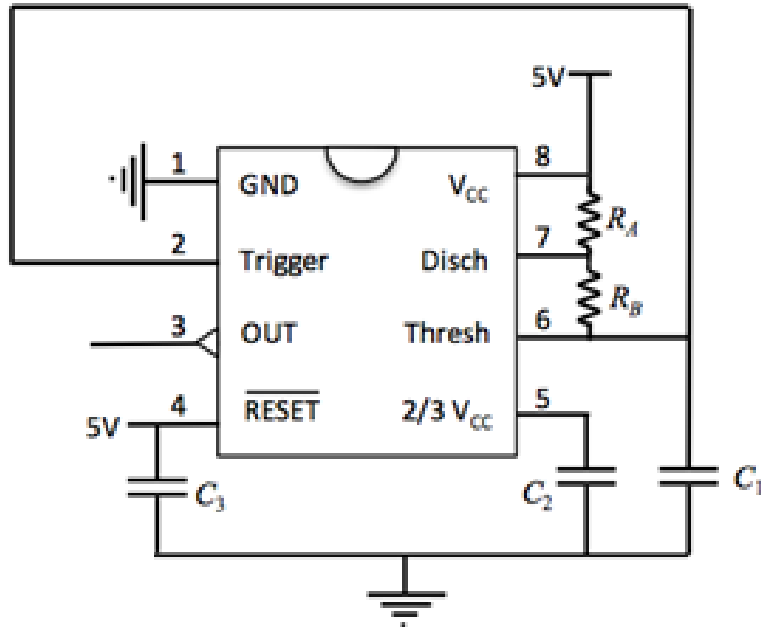


$$R_A = 30k\Omega \quad R_B = 10k$$

$$C_1 = C_2 = C_3 = 0.1\mu F$$

Frequency = ?

Duty cycle = ?

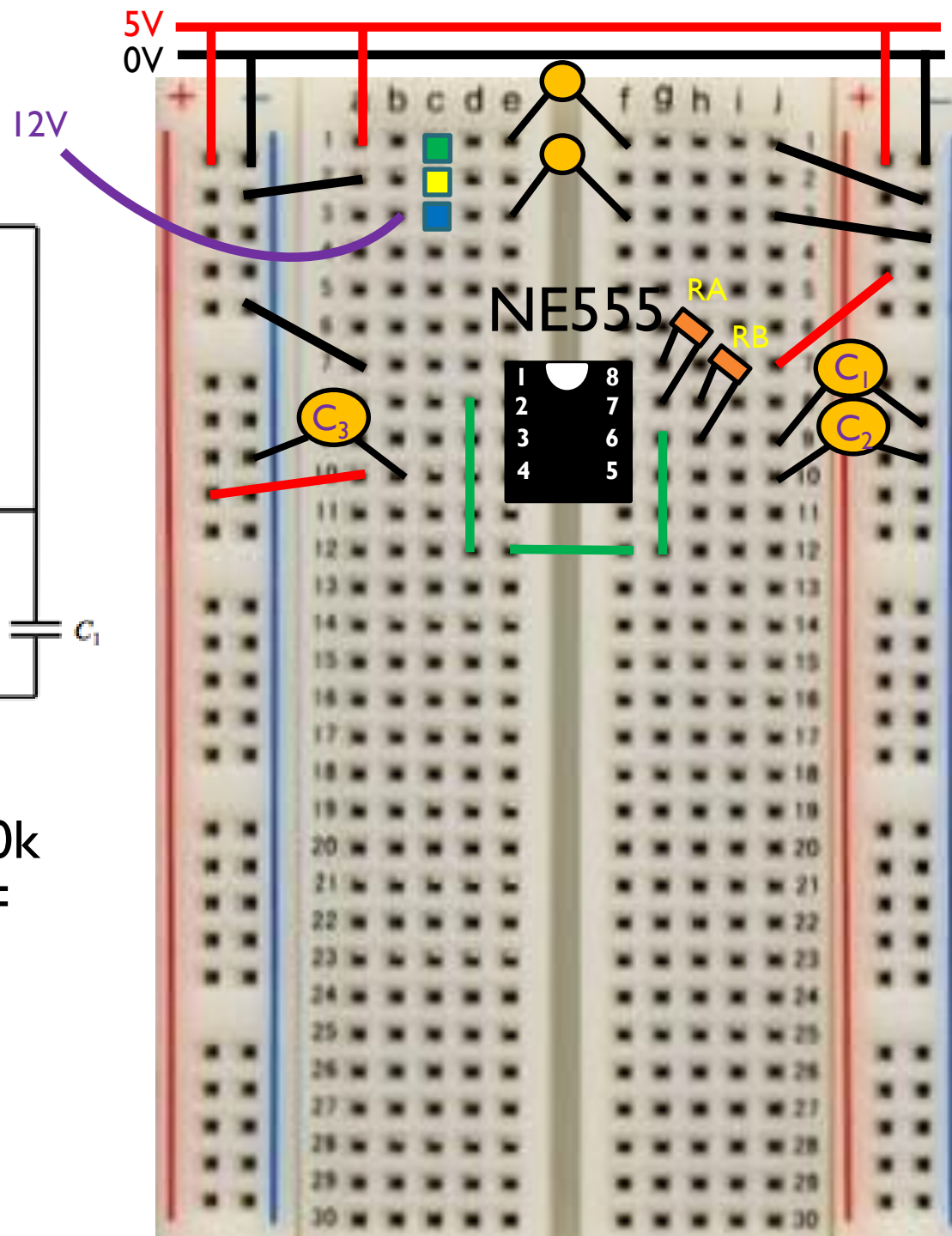


Schmitt Trigger 74HC14


- Practical output of timer:



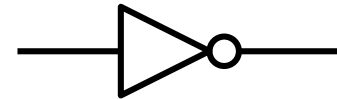
- Solution: Schmitt Trigger
- Straighten up the pulse



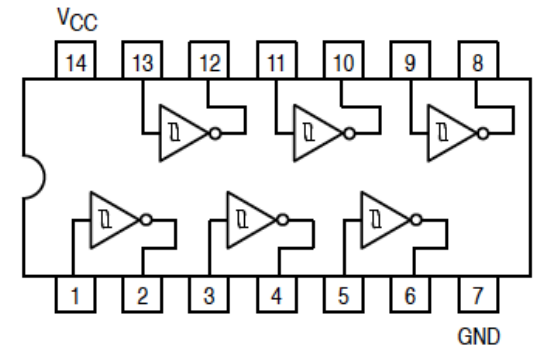- There are 6 Schmitt Triggers and you only need to use one **14 pins, 6 pairs**
- The V_{CC} (positive supply) and GND has to be connected to power for proper function **1, 2, 7, 14**



+

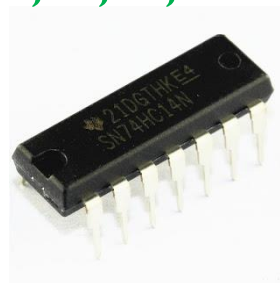

=

****The output is inverted**



Lab#02: Experiment 4

Use a variable resistor to replace R_A and R_B

