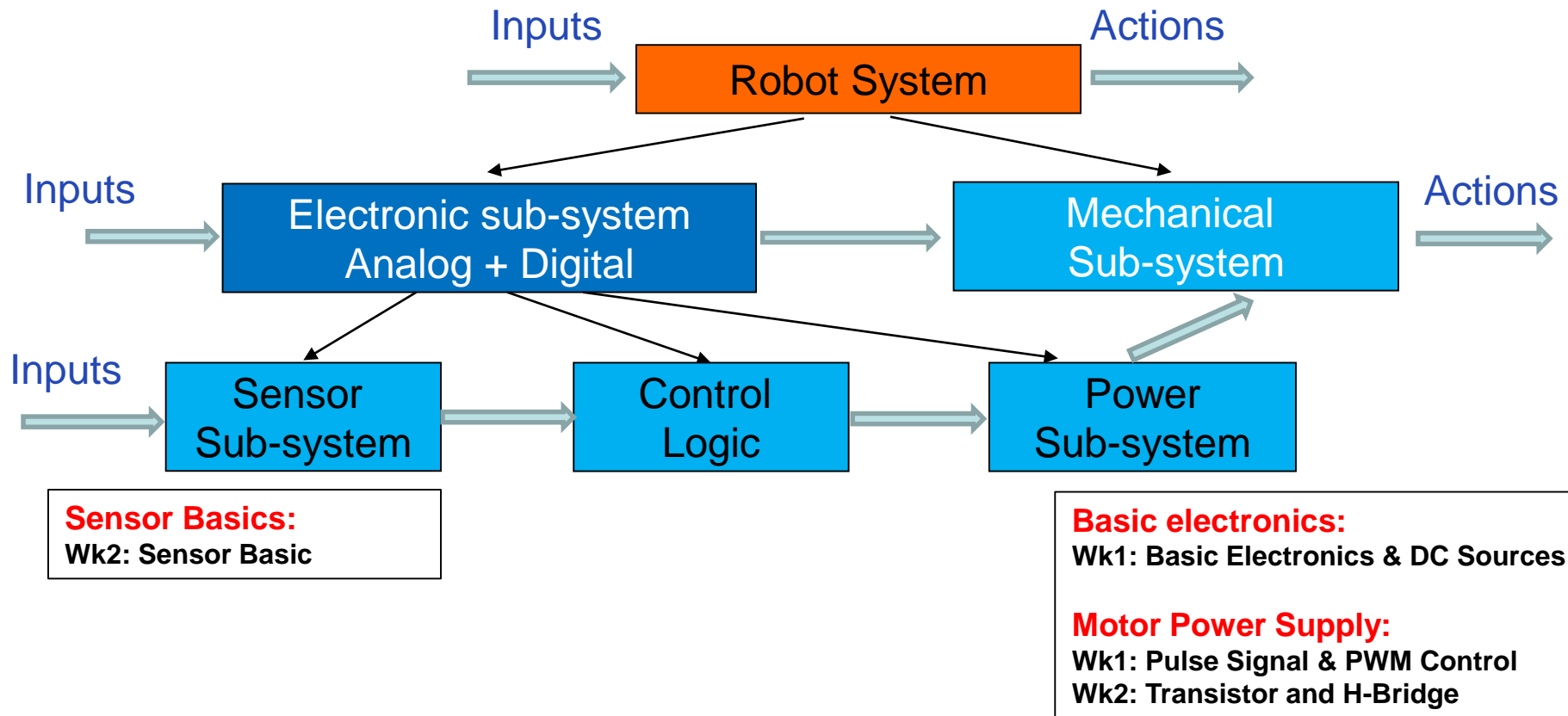


ELEC 1100: Introduction to Electro-Robot Design

Lecture 3: Transistors + H-bridge + Sensors

CHEN Wei, Dept. of ECE, HKUST

ELEC1100 ROADMAP



LAST LECTURE

❖ A comparator compares 2 binary numbers

$A (=A_3A_2A_1A_0)$ and $B (=B_3B_2B_1B_0)$

❖ If $A < B$, the pin $A < B$ will go high and so on

❖ Suppose the number A comes from the counter 74HC161 and starting from 0000


❖ By inputting a fixed number to B , we can control the duty cycle at output of $A < B$

$O_{A < B}$ output



$B=0$




$B=4$

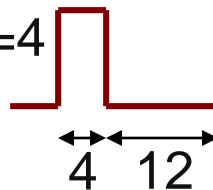

$B=15$

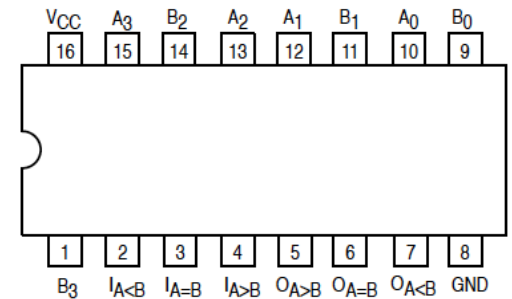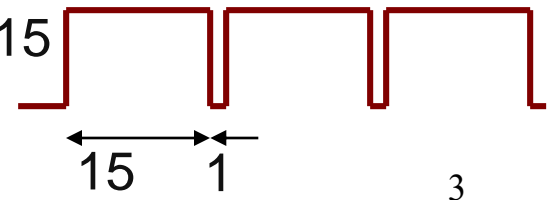


LAST LECTURE

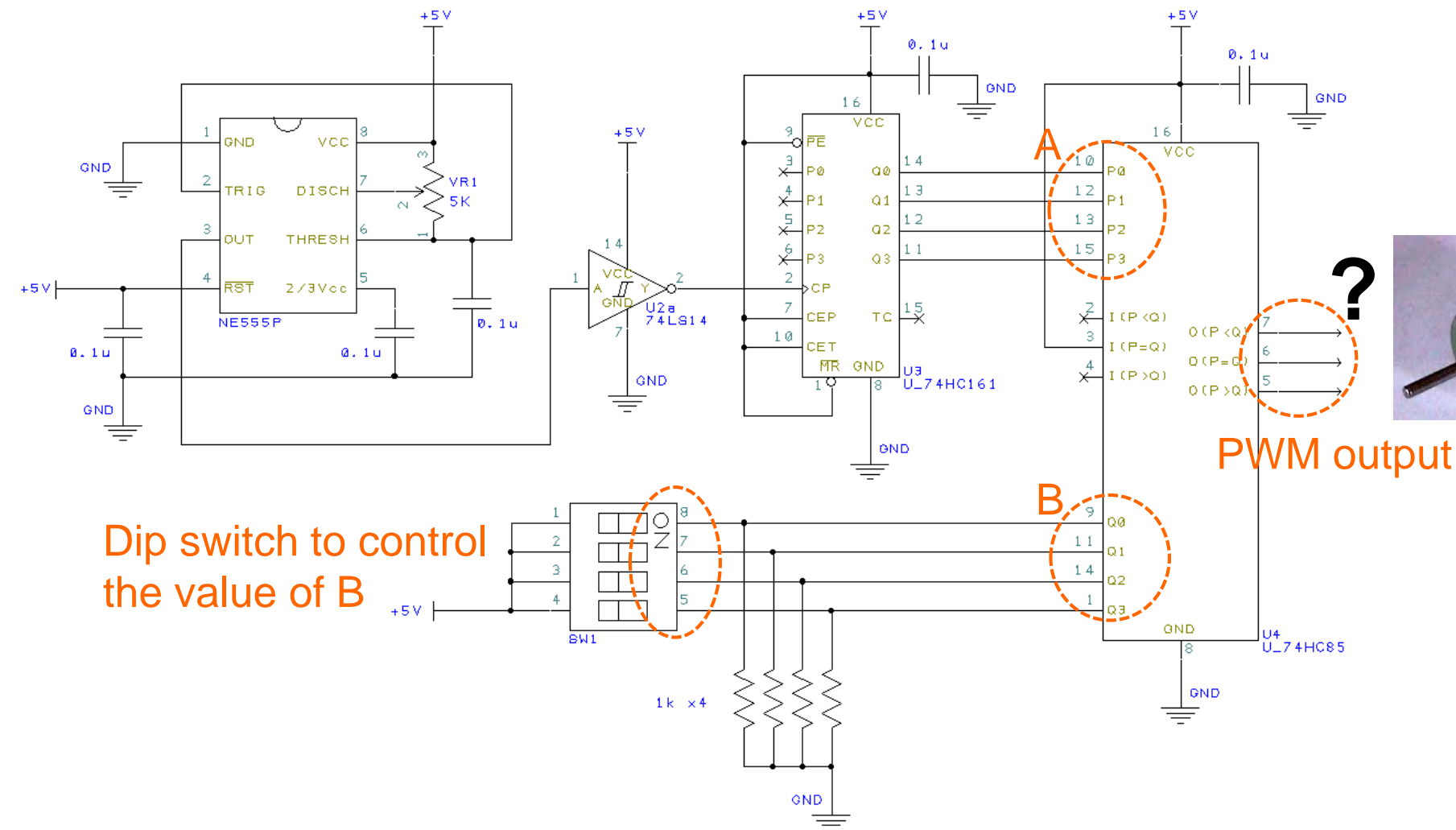

INTERFACING PWM CIRCUIT TO THE MOTOR

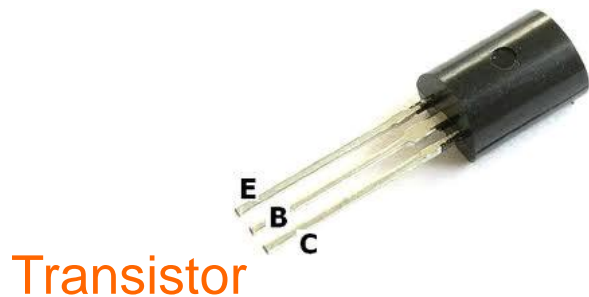- ❖ Brushed motors usually require very high current to drive it.
Thus, the driving signal needs to be amplified by a transistor
- ❖ A transistor is a 3-terminal device that can be viewed as a electronic switch
- ❖ The conductivity between two of the terminals is controlled by the third terminal



analogy

A SHORT HISTORY OF TRANSISTOR

- ❖ Invented in Bell Labs by William Shockley, John Bardeen and Walter H. Brattain



- Shockley: “one of the century’s most important scientists”, Times Magazine
 - Bardeen: won Nobel Prize twice !
 - The three of them won the 1956 Nobel Prize in Physics for inventing the transistor
- ❖ Bardeen and Brattain made the breakthrough and Shockley put a nice ending
 - ❖ However Shockley was not a good leader. Brattain refused to work for him anymore and Bardeen just quit

THE SILICON VALLEY




- ❖ Shockley moved to Stanford and founded Shockley Semiconductors in Palo Alto, the beginning of Silicon Valley



- ❖ Shockley hired the brightest scientists and engineers (e.g. Gordon Moore and Bob Noyce, founders of Intel) who founded many companies after they left Shockley

THE FIRST TRANSISTOR

❖ Resemble the schematic shown earlier

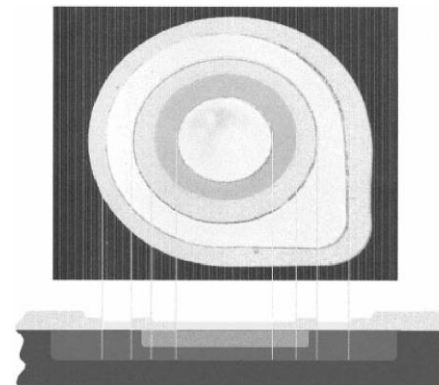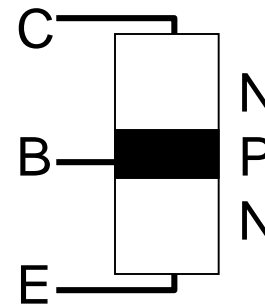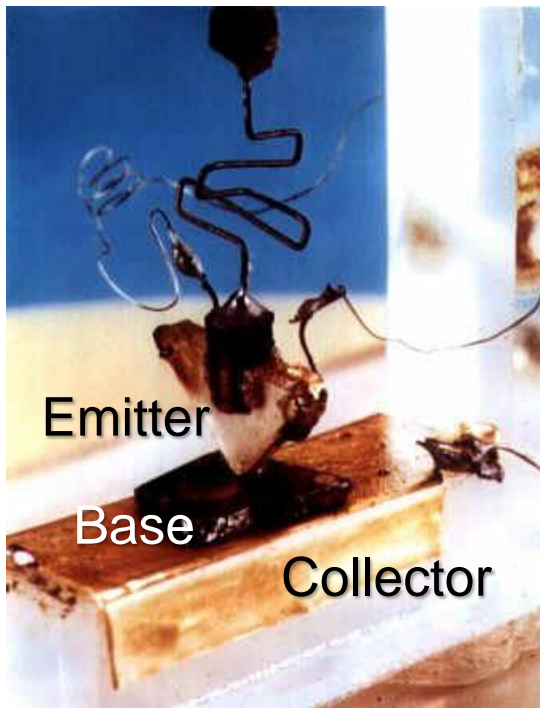


Modern planar
transistors



BIPOLAR JUNCTION TRANSISTOR (BJT)


❖ There are two types of standard BJT

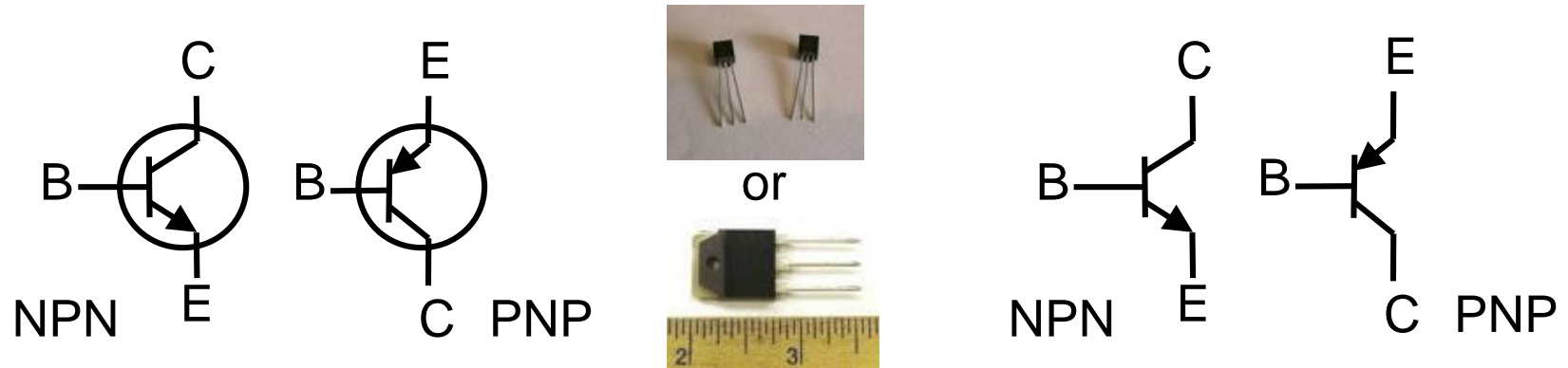

❖ The leads are labeled Collector (C), Base (B) and Emitter (E)


➤ The N and P refers to the material type that is used to construct the transistor

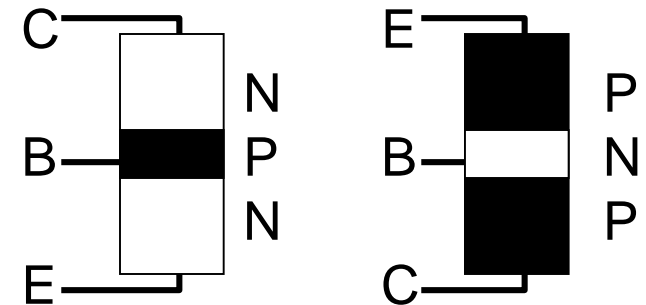❖ Detail operation will be covered in other courses




TRANSISTORS AS SWITCHES

❖ Simple equivalent of NPN transistors

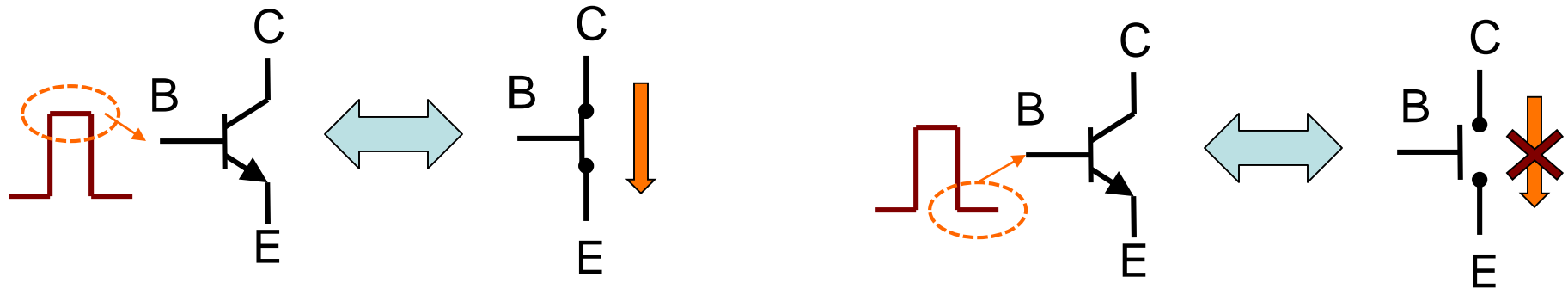


❖ Simple equivalent of PNP transistors

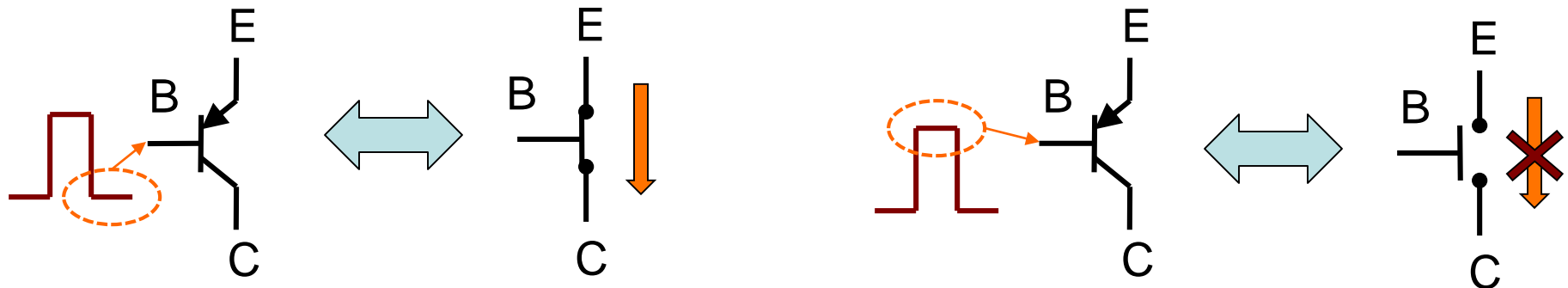


MORE REALISTIC OPERATION OF A BJT

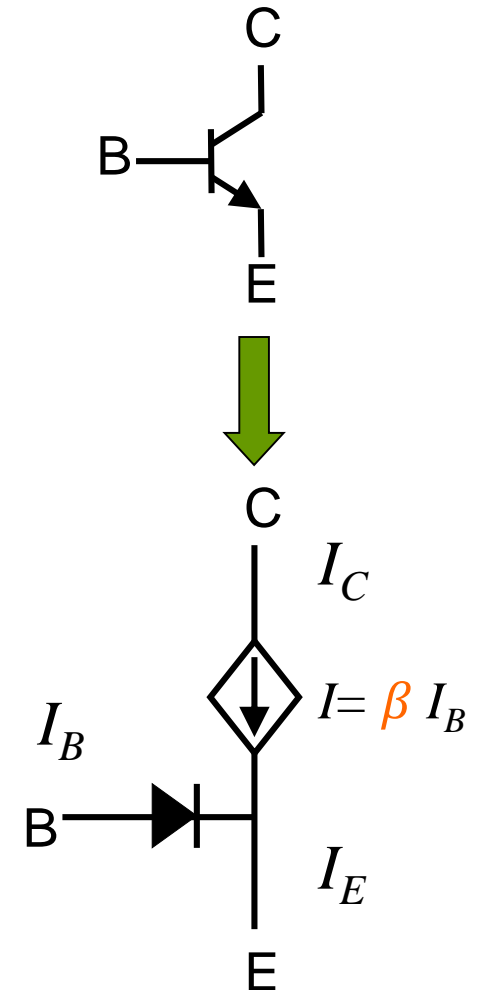- ❖ The B-E terminal of a BJT is actually behaving like a diode
- ❖ A base current I_B flows only when the voltage V_{BE} across the base-emitter junction is about $0.7V$
- ❖ Collector current is proportional to the base current, i.e., $I_C = \beta I_B$ where β is the current gain.
- ❖ β is in the range of 20-200, leading to an amplification of current




DIODE CIRCUIT ANALYSIS

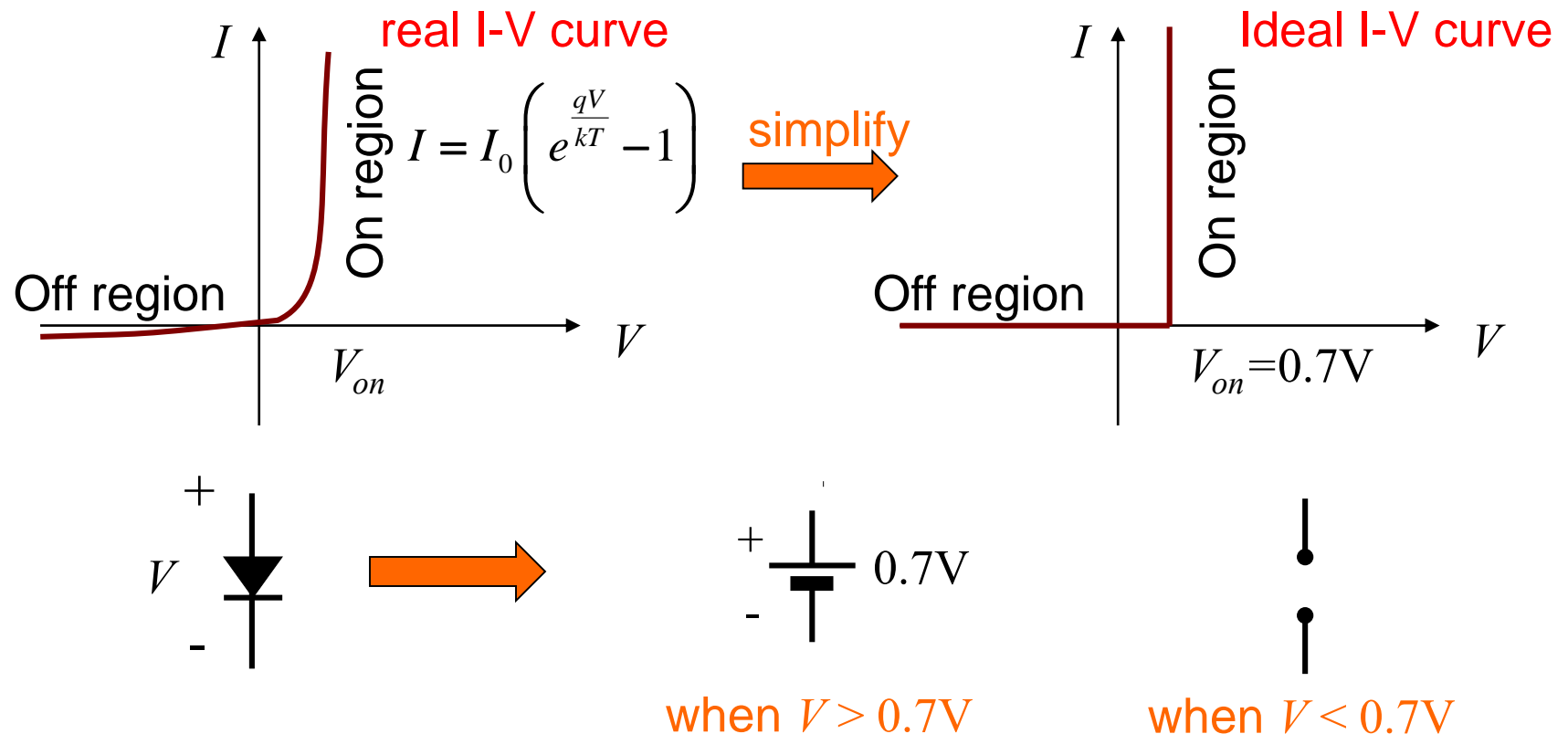- ❖ To understand transistor operation, one needs to first understand diode circuits



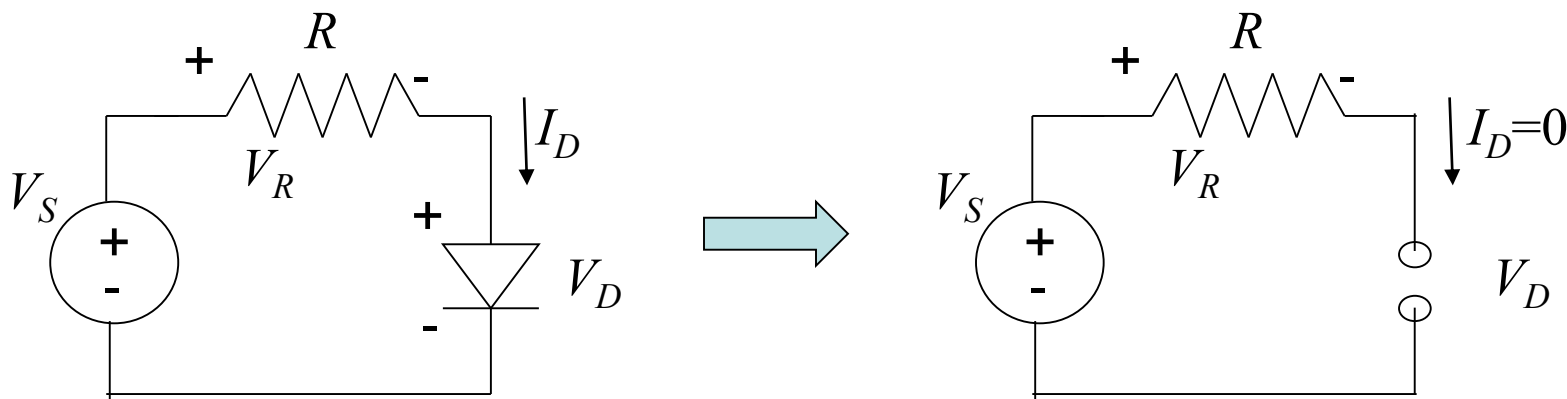EXAMPLE OF DIODE CIRCUITS

- ❖ Assume off region, replace it with the equivalent model




$$I_D = 0 \Rightarrow V_R = 0 \Rightarrow \boxed{V_D = V_S}$$

- ❖ If $V_S < 0.7\text{V}$, the assumption is correct and answer found
- ❖ Otherwise, assumption is wrong and we try the other case

CURRENT THROUGH THE DIODE

❖ When $V_S > 0.7V$

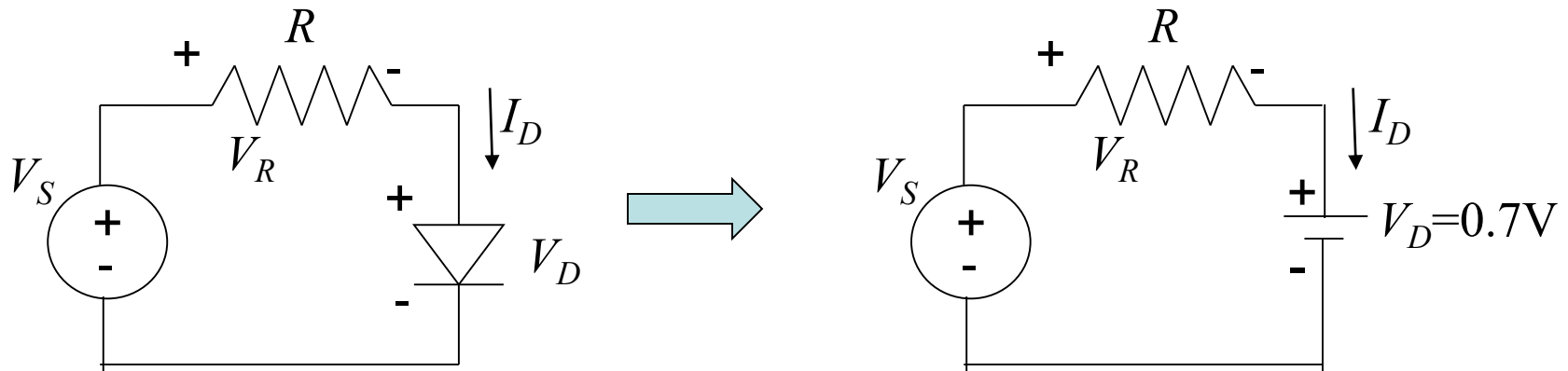



❖ We can obtain $V_S - 0.7 = V_R \Rightarrow I_D = \frac{V_S - 0.7}{R}$

❖ If the condition is incorrect (or $V_S < 0.7V$), $I_D < 0$

❖ It is important to have a resistance in series with a diode, or the current can be very large

CIRCUIT WITH TWO DIODES

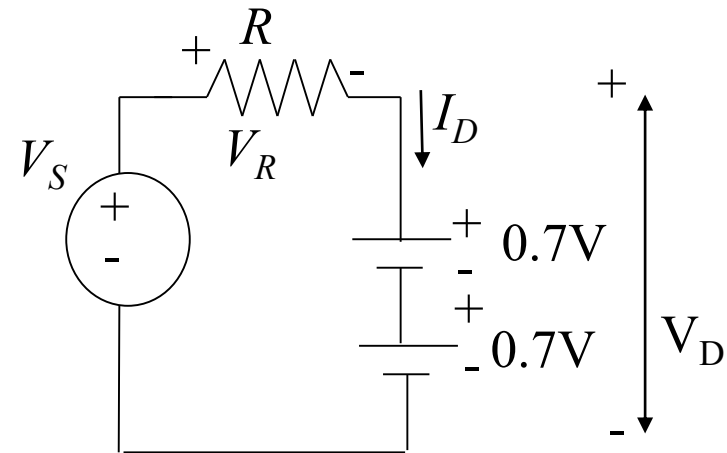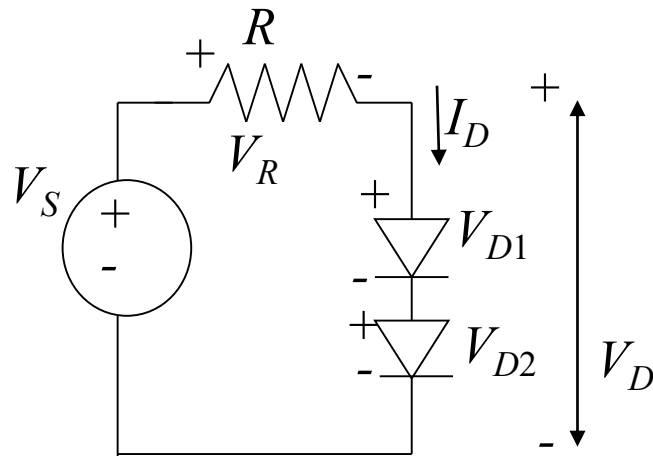❖ Circuit with two diodes can be solved in the same approach



❖ It is simple and leave it to you as an exercise


BACK TO TRANSISTOR

- ❖ A resistor is always needed at the base to avoid a very high current

$$I_B = \frac{V_{IN} - 0.7}{R_B}$$


- $I_B = 0$, transistor is off
- I_B small: active mode with transistor partially on
- I_B large: transistor fully on

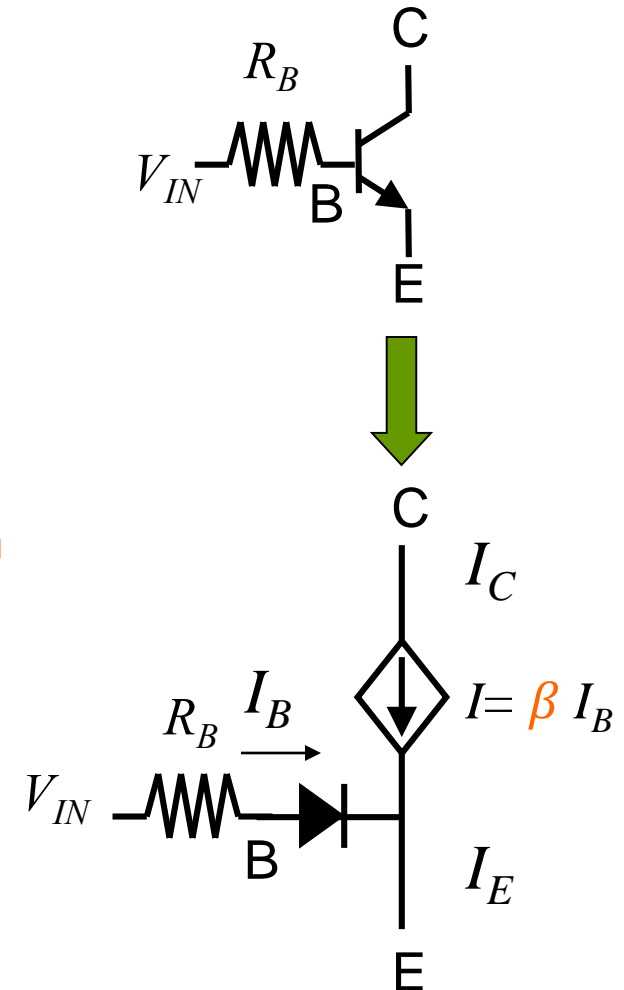- ❖ As long as the input voltage V_{IN} is larger than $0.7V$, you can consider the transistor is on (either partially or fully)



CIRCUIT EXAMPLE: LIGHT ACTIVATED SWITCH

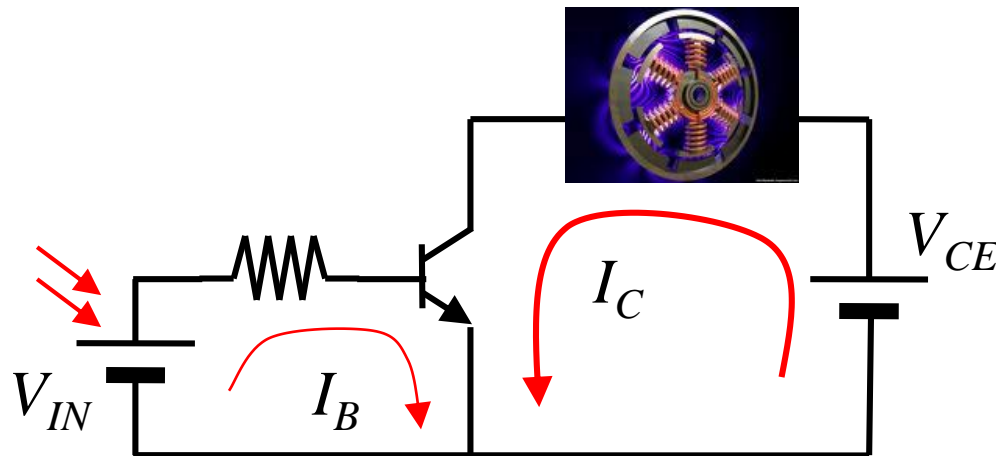
- ❖ Consider a circuit to turn on a fan under strong light
- ❖ You may simply connect the fan to a solar cell, but the solar cell is not powerful enough to drive the motor
- ❖ Consider using a solar cell to give the V_{BE} of a NPN transistor



- Can use a small power to control the delivery of a large power
- A transistor can be used as an “amplifier”


PNP TRANSISTOR

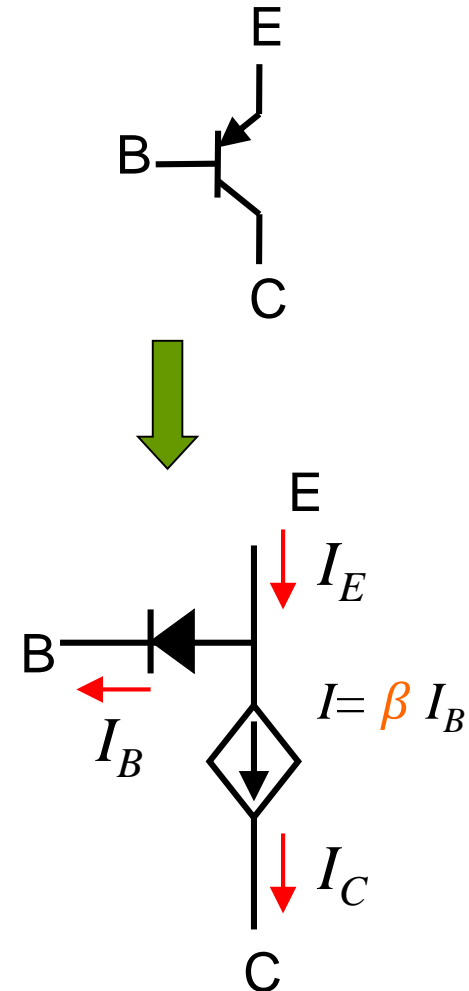- ❖ PNP transistor is similar to NPN, but the diode is between the power supply and the input
- ❖ As long as $V_{BE} < -0.7\text{V}$, you may consider the transistor to be on
- ❖ Allow a switch to be turned on with low voltage



CIRCUIT EXAMPLE WITH PNP TRANSISTORS

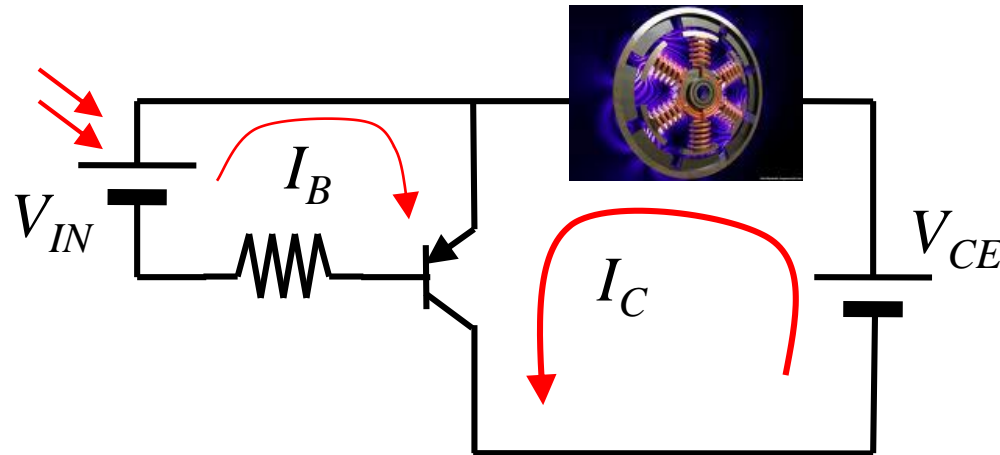
- ❖ For the same circuit to turn on a fan under strong light using PNP transistor looks like the following:




- ❖ The performance is exactly the same as the NPN case

SUMMARY

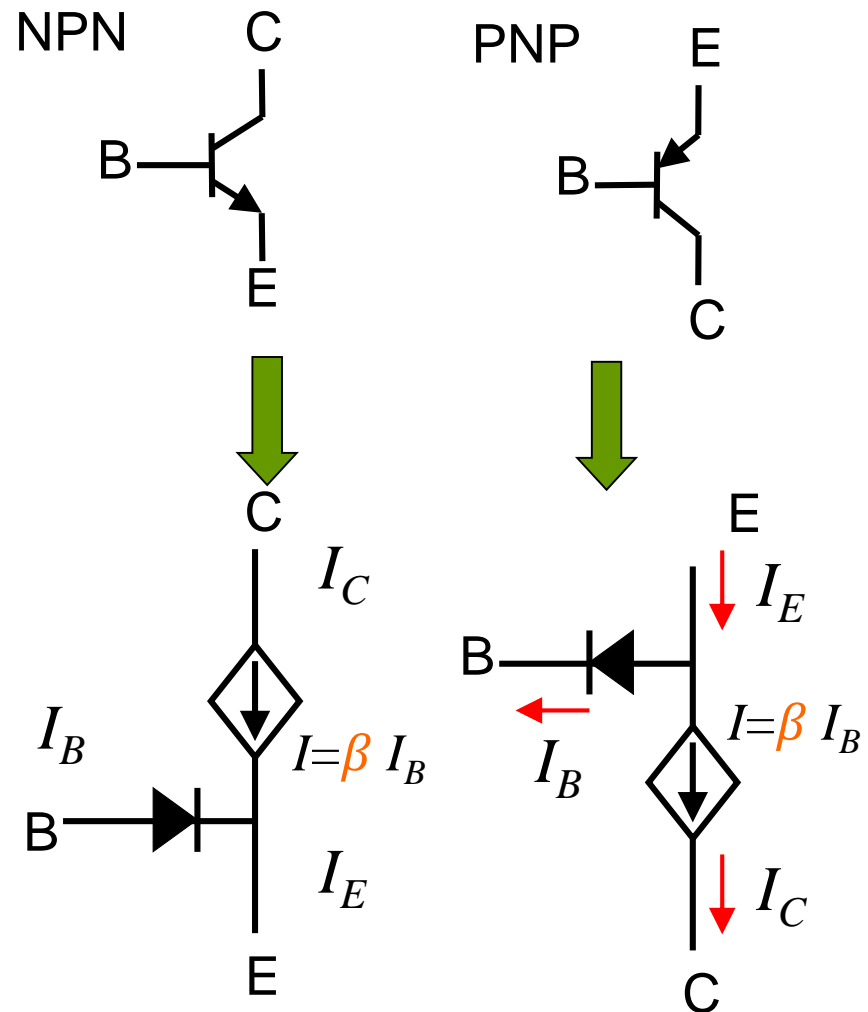
- ❖ NPN and PNP transistors and their equivalent circuits
- ❖ Calculating diode current by assuming it is either a battery or an open circuit
- ❖ Transistors can be used as a switch or an amplifier



SPECIFICATION OF BJT CHARACTERISTICS

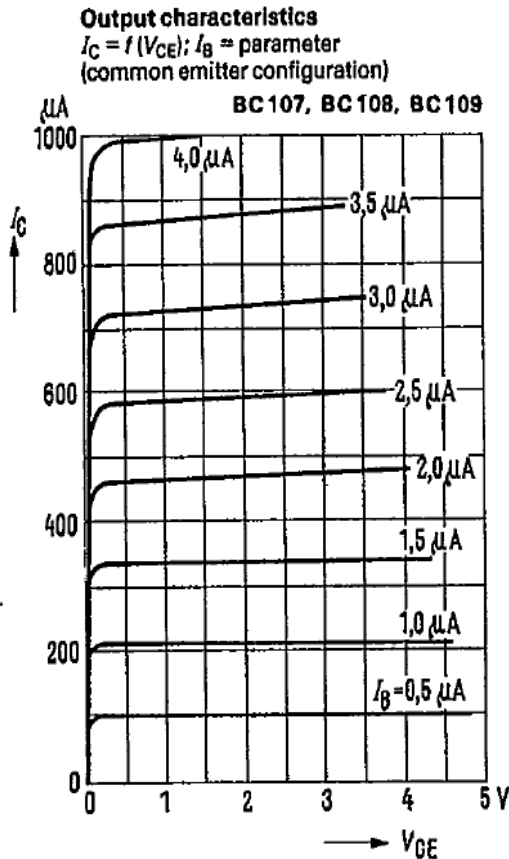

Current Control


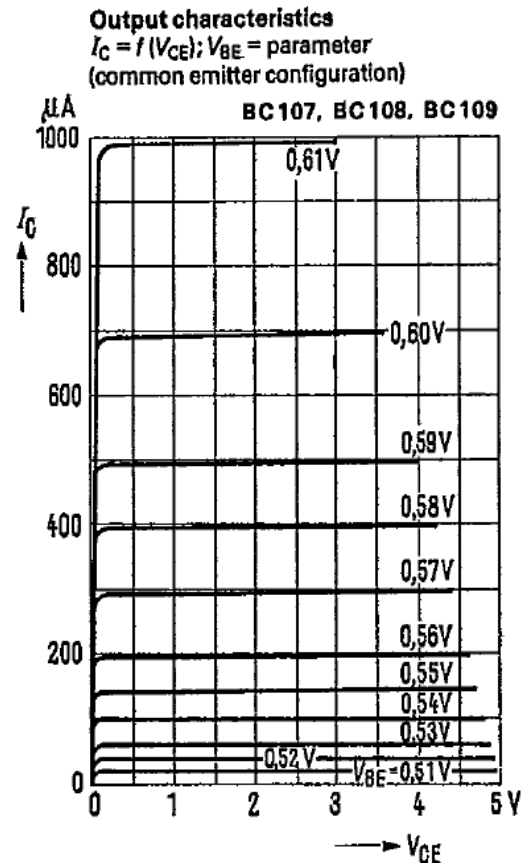


Voltage Control

- I_C is more or less proportional to base current
- I_C is non-linearly dependent on V_{BE} and very sensitive to it
- As a result, current control is more easy to perform

SWITCH VERSUS AMPLIFIER

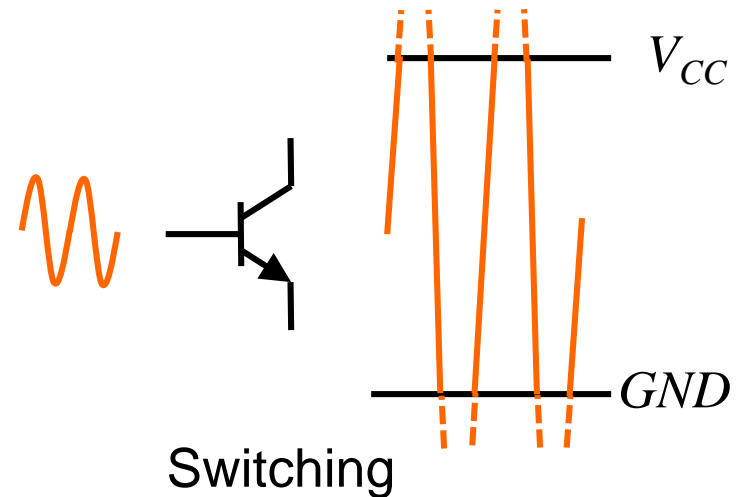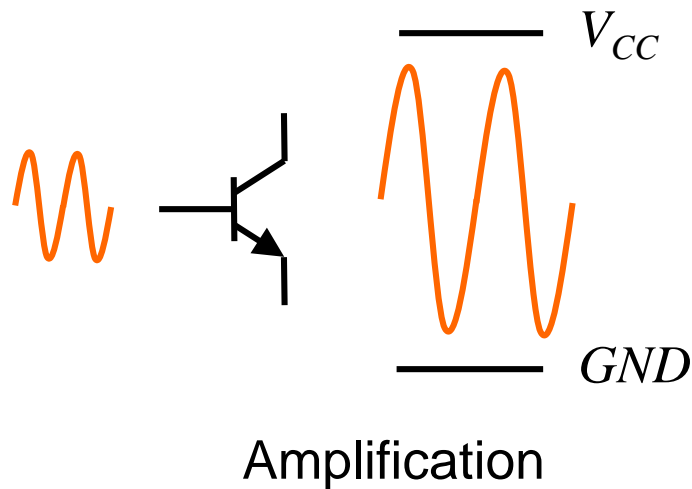
- ❖ Consider an AC signal input to an amplifier with different gain



- ❖ For large input signal, an amplifier becomes a switch
- ❖ Many applications like audio and sensor signal processing require a transistor to operate in the amplification mode

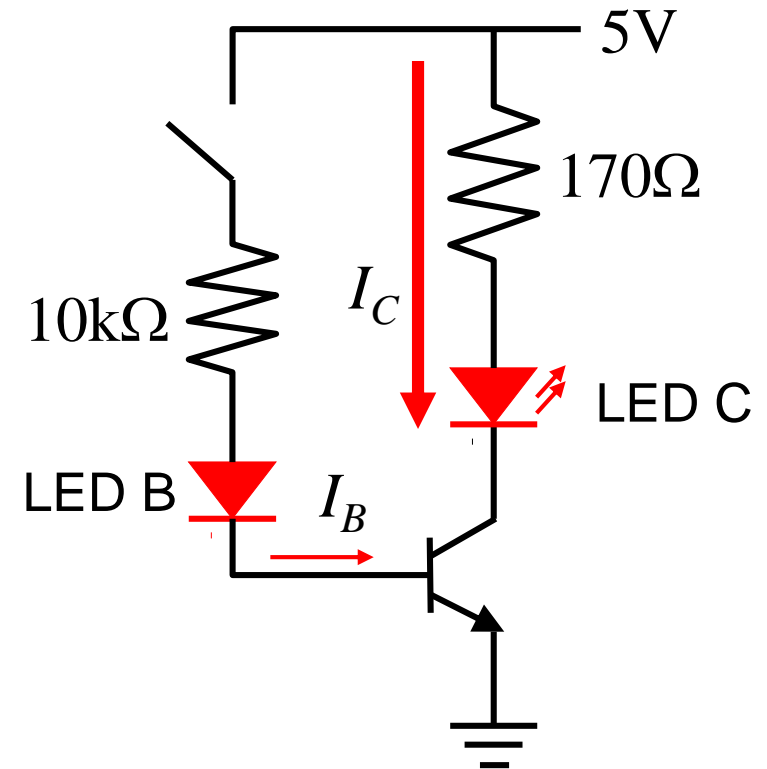
EXAMPLE OF BJT CIRCUIT

- ❖ When the switch is Open, there is no collector current
 - ❖ When the switch is Closed, a small current flows into the base of the transistor, which is just enough to make the LED B glow dimly
 - ❖ The transistor amplifies this small current to allow a large current to flow from its collector to its emitter that makes LED C to light brightly
- Question: what is the maximum possible collector current?




MAXIMUM AND ACTUAL COLLECTOR CURRENT

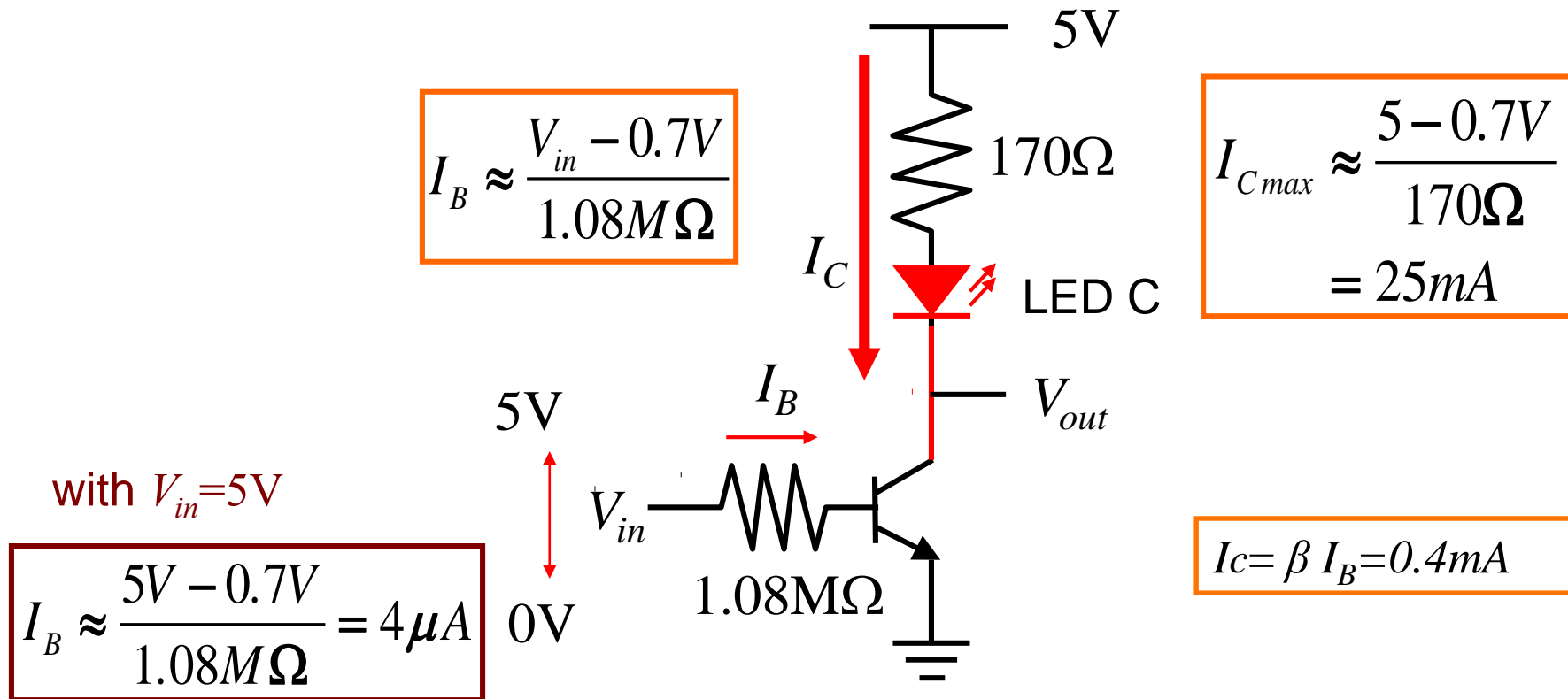❖ Consider the following circuit, assuming $\beta = 100$




AT HIGH BASE CURRENT

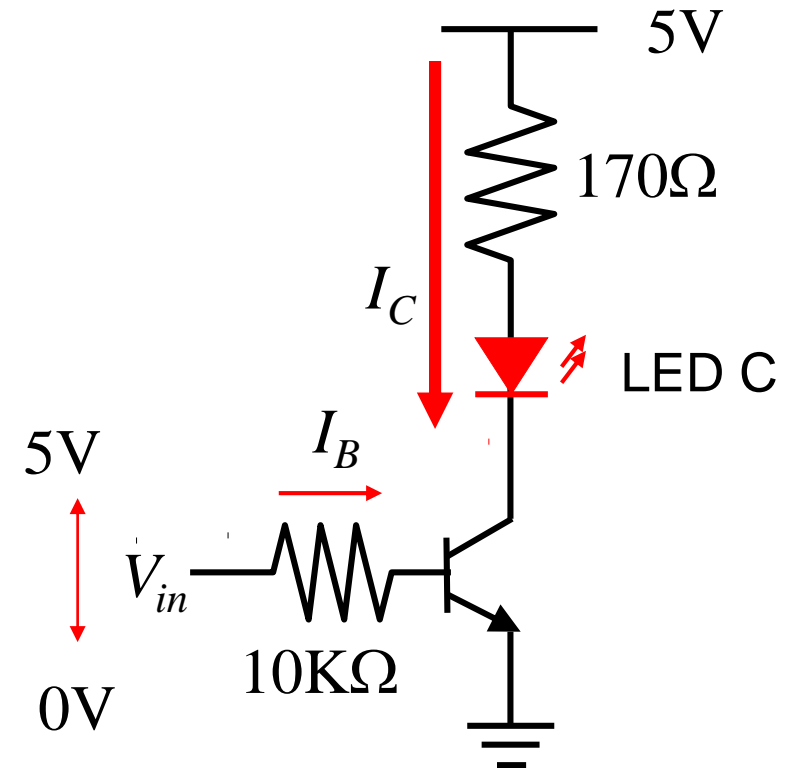- ❖ In the given figure, $I_B \approx 0.43\text{mA}$
- ❖ With $\beta = 100$ and using the given relationship, $I_C = I_B \times \beta = 43\text{mA}$
- ❖ This I_C is higher than the 25mA allowed thus a gain of $\beta = 100$ is not possible
- ❖ When the transistor is fully turned on with high I_B , we call the transistor is saturated
- ❖ The transistor behaves as a switch





MORE EXAMPLE

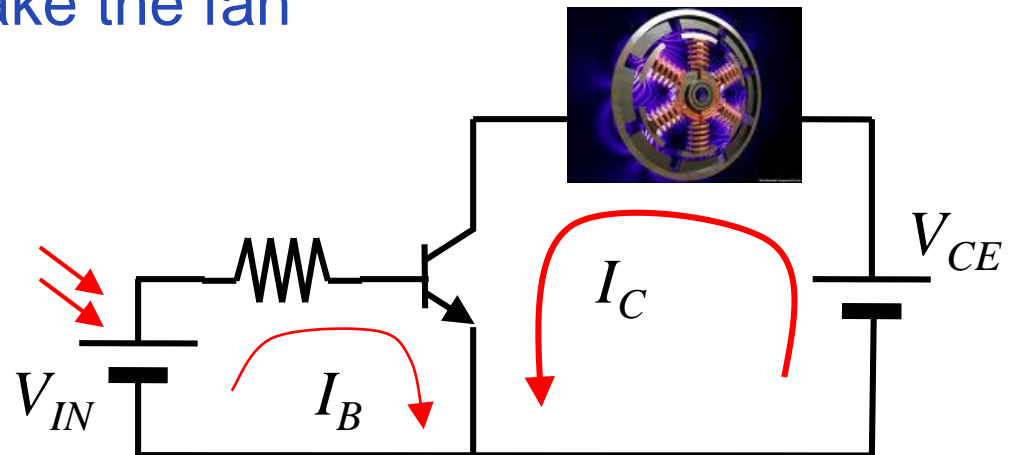- ❖ How to make the light controlled fan behaves like a switch that whenever there is light, the fan is fully on?
- ❖ How to make the speed of the fan proportional to the light input (i.e. stronger light would make the fan turn faster)?




H-BRIDGE CIRCUIT (SWITCHES)

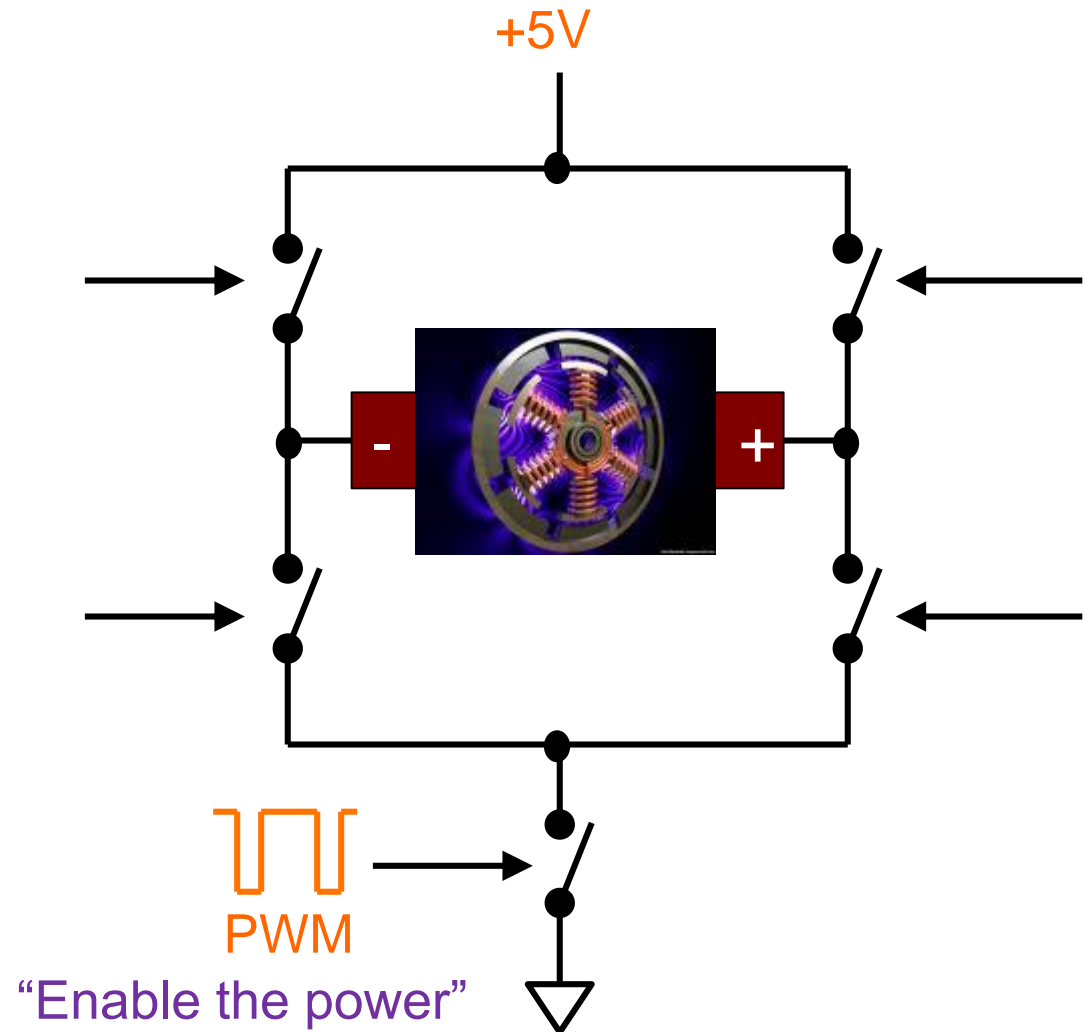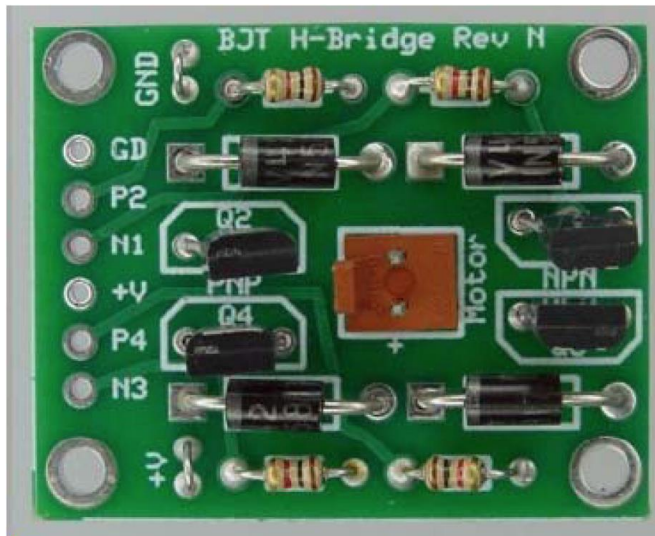- ❖ It is the circuit to control both the motor direction and speed
- ❖ Use a direction (DIR) pin to control the switches



H-BRIDGE OPERATION SUMMARY



Command	R1	R2	R3	R4
Coast/Roll/Off	GND or disconnected	+VDC or disconnected	GND or disconnected	+VDC or disconnected
Forward:	GND or disconnected	GND	+VDC	+VDC or disconnected
Reverse:	+VDC	+VDC or disconnected	GND or disconnected	GND

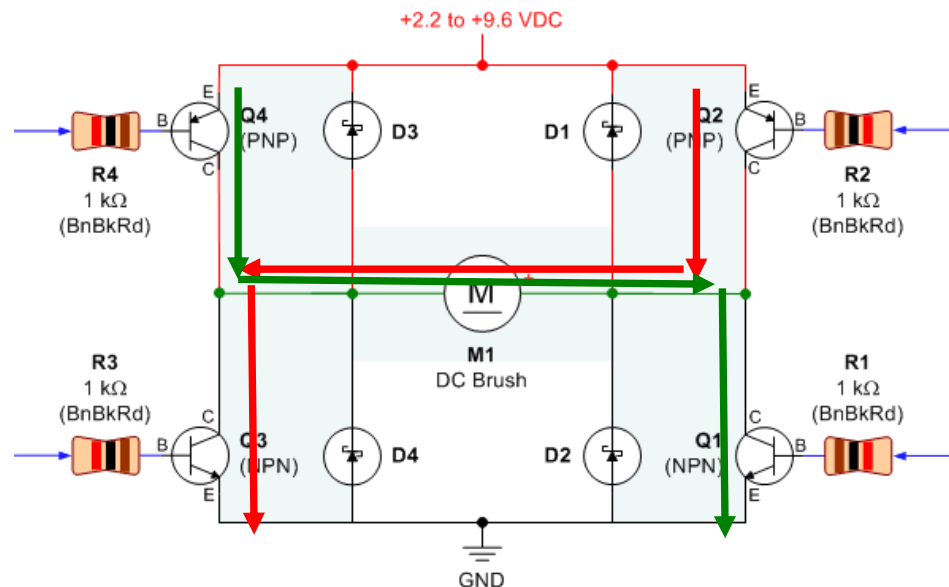

H-BRIDGE CIRCUIT (TRANSISTORS)


- ❖ It is the circuit to control both the motor direction and speed

Connect to either 5V or 0V

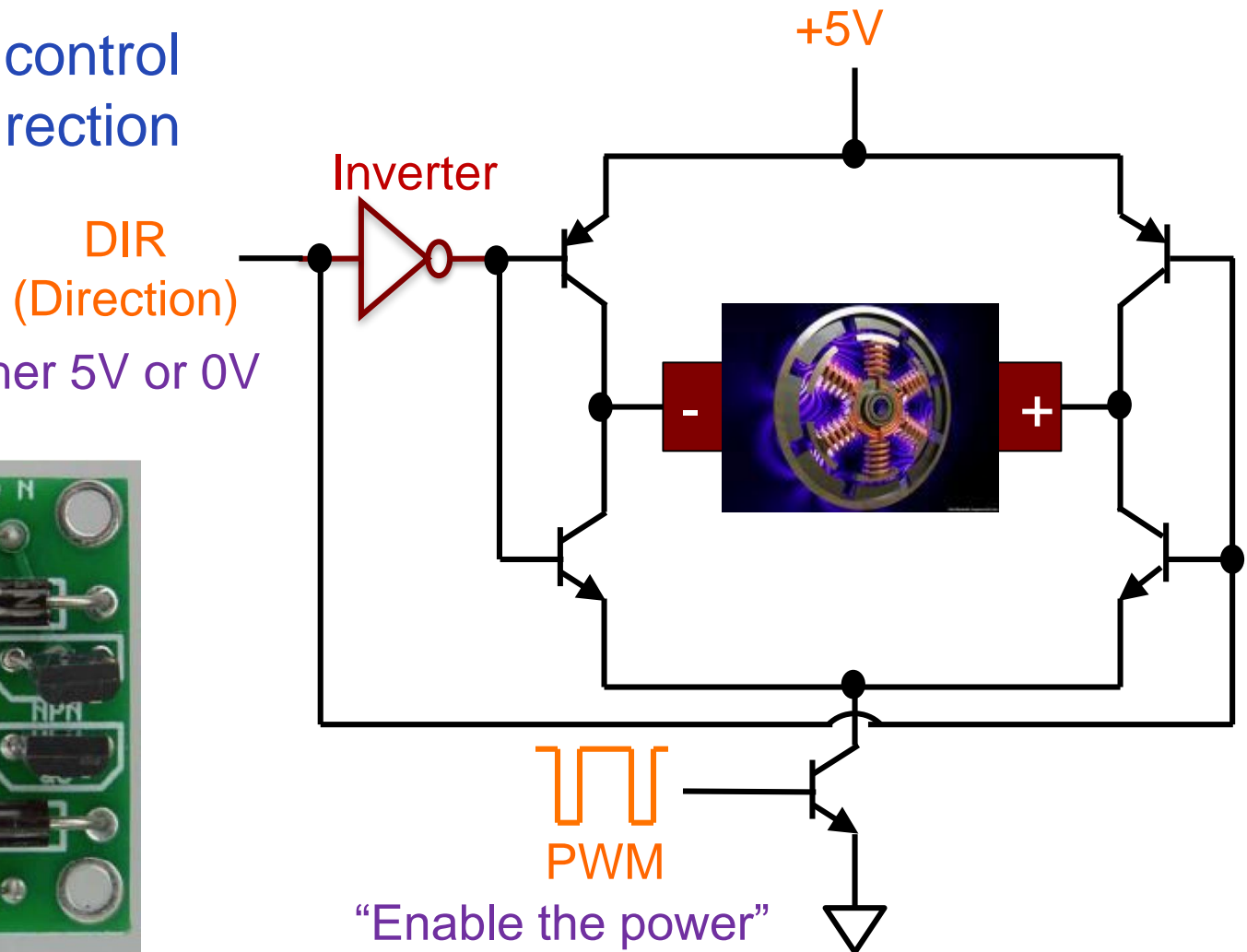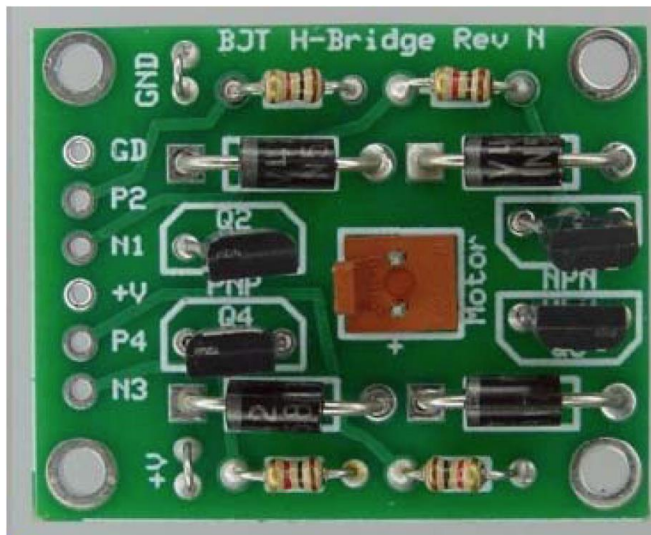


H-BRIDGE IC – L293B

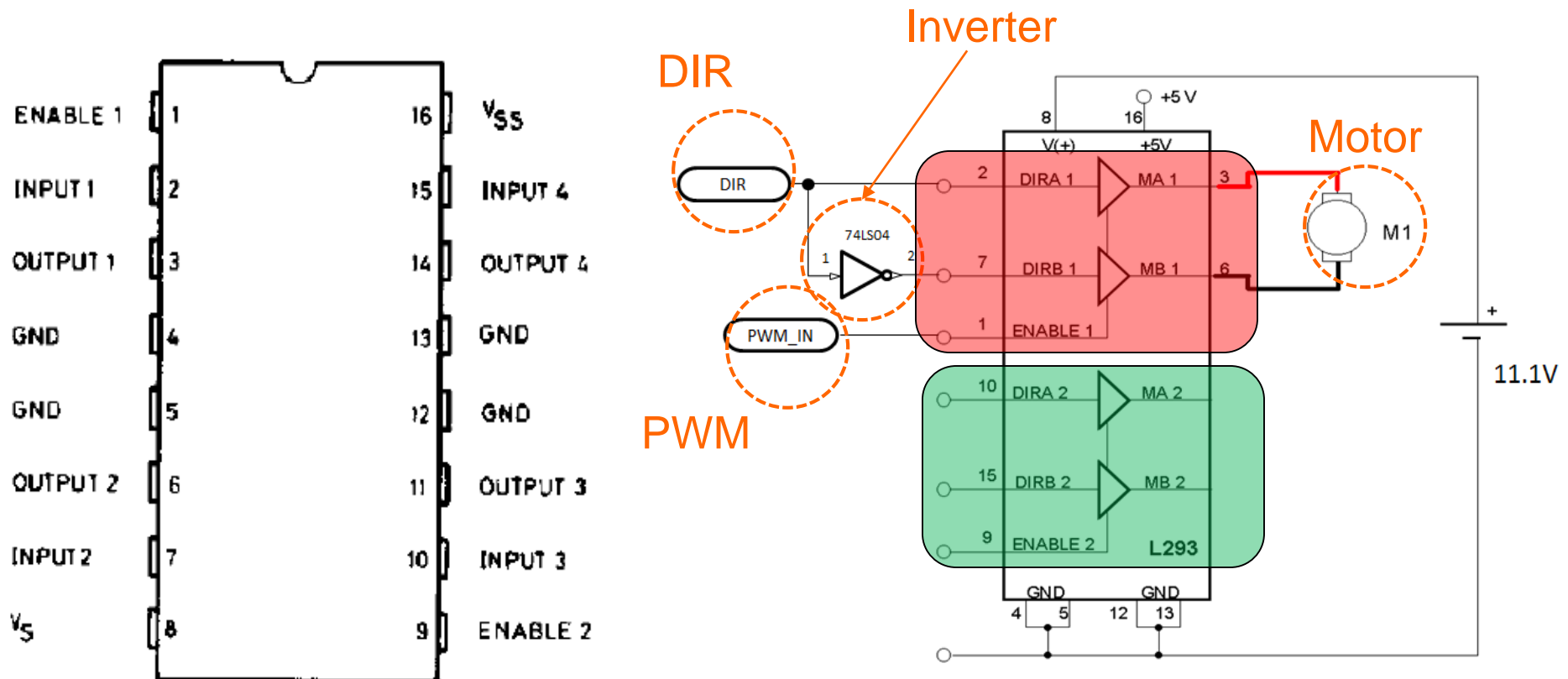- ❖ To simplify your task without using transistors, you may use the H-bridge IC in your lab and project




SUMMARY

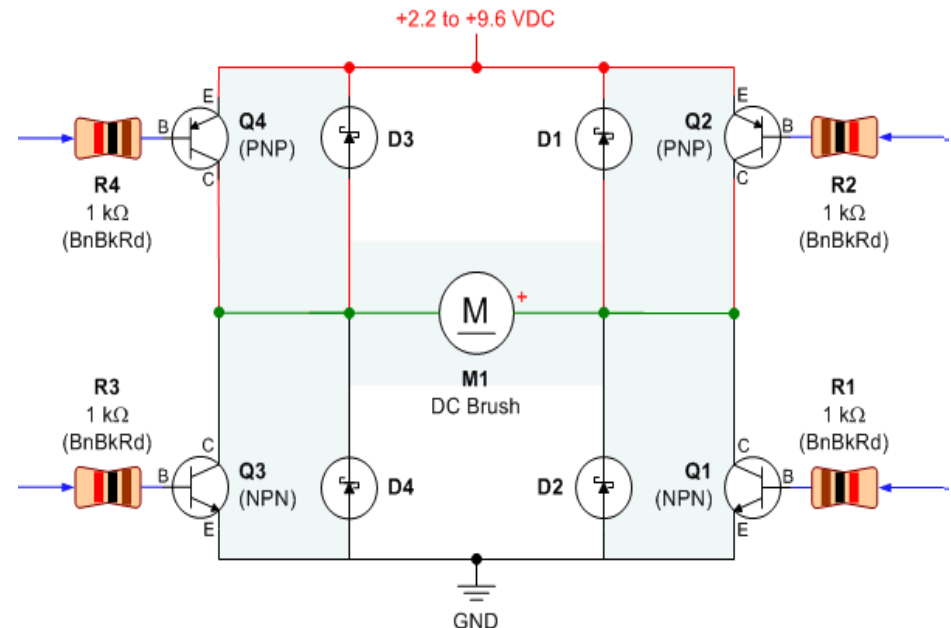- ❖ A transistor can work in the switch mode or amplification mode
- ❖ A switch mode happens when the input current is very high that saturates the transistor
- ❖ Transistors can be used to construct a H-Bridge to drive a motor













WHAT IS A SENSOR?

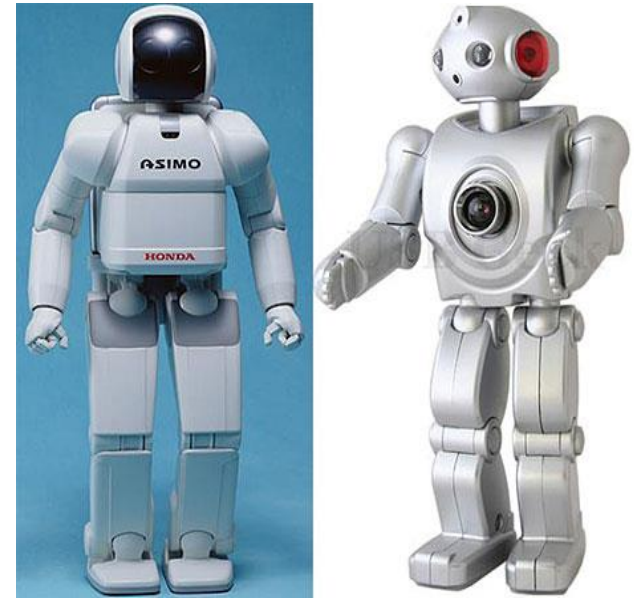- ❖ A device that measures or detects a real-world condition, such as motion, heat or light and converts the condition into an analog or digital representation
- ❖ It is the equivalent of eyes, ears and skin of a Robot to find out the environment it is situated
- ❖ Made up of camera, microphone, gyroscope etc.



TYPES OF SENSOR

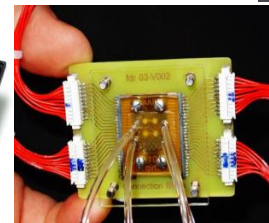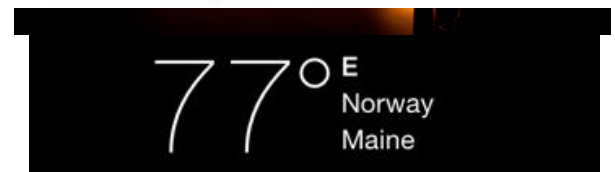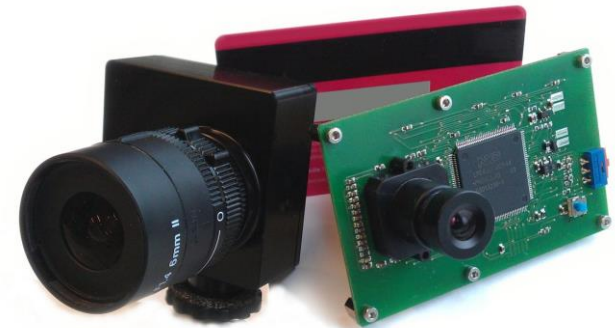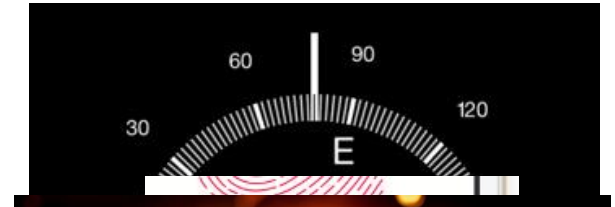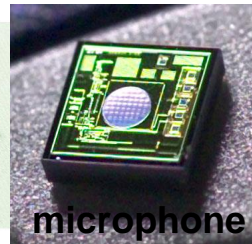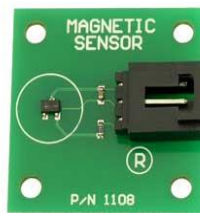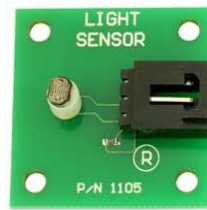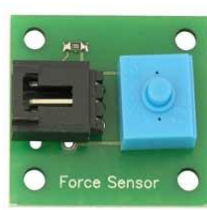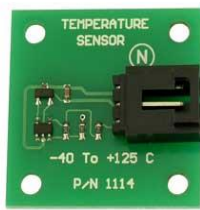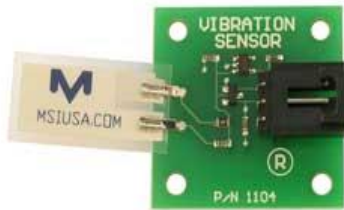

chemical sensor image sensor biosensor


gyroscope



Fix iPhone
Proximity Sensor
Not Working

OPTICAL SENSORS

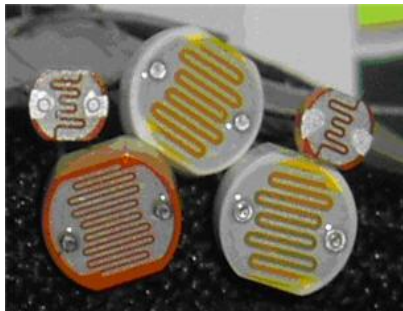
- ❖ Example of common optical sensors are light sensitive resistor (CdS) and photodiode
- ❖ Optical sensors can be combined with light sources to produce line sensors to detect position (the one you used in your lab)



CdS




Photodiode

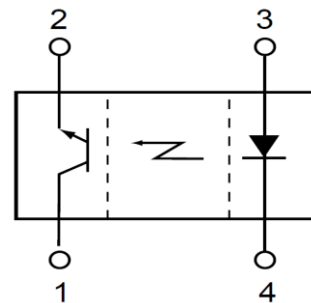




Line Sensor

LINE SENSORS

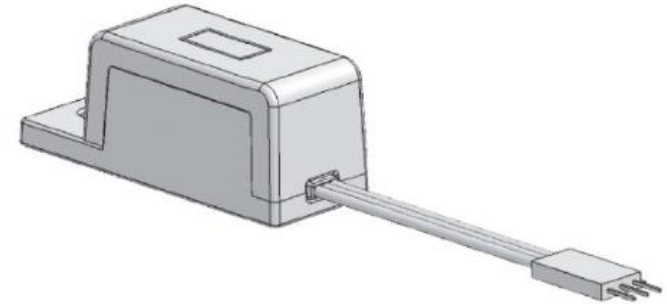- ❖ The Navidroid include an infrared light sensor and an infrared LED
- ❖ The LED illuminates the surface and the light sensor picks up the infrared radiation
- ❖ Light-colored surface will reflect more light than dark surface
- ❖ Therefore a dark line in a pale surface or a pale line in a dark surface can be detected





LINE SENSORS

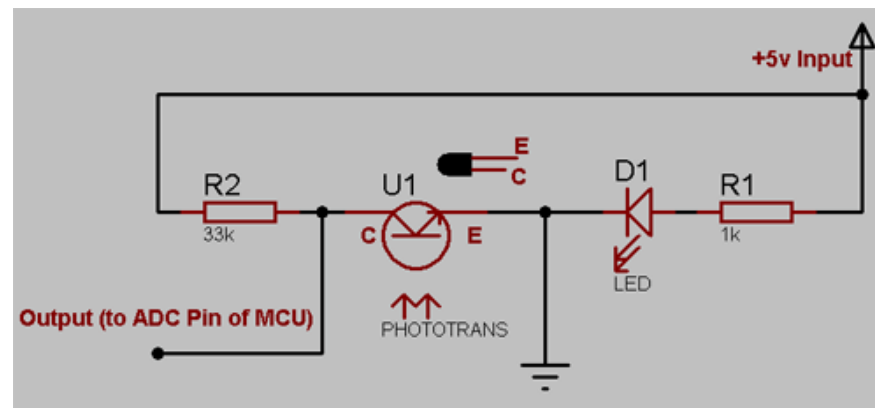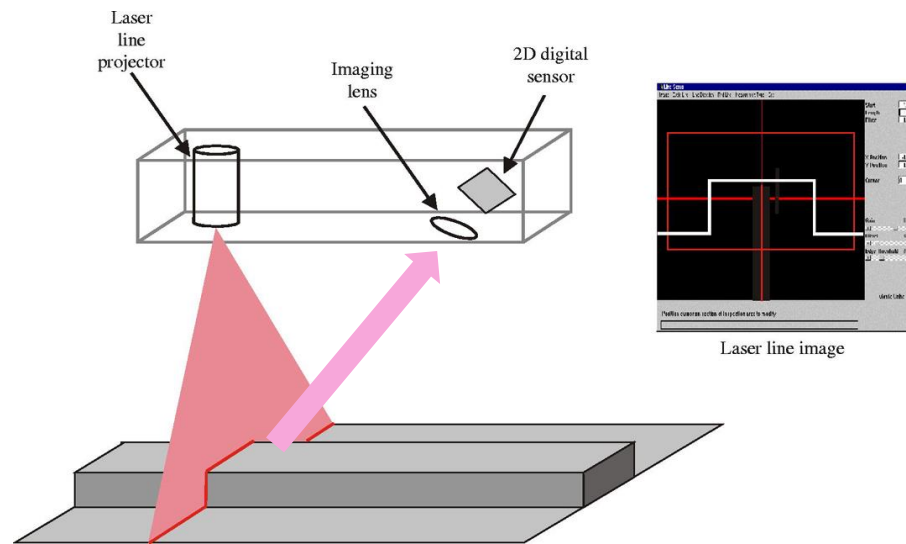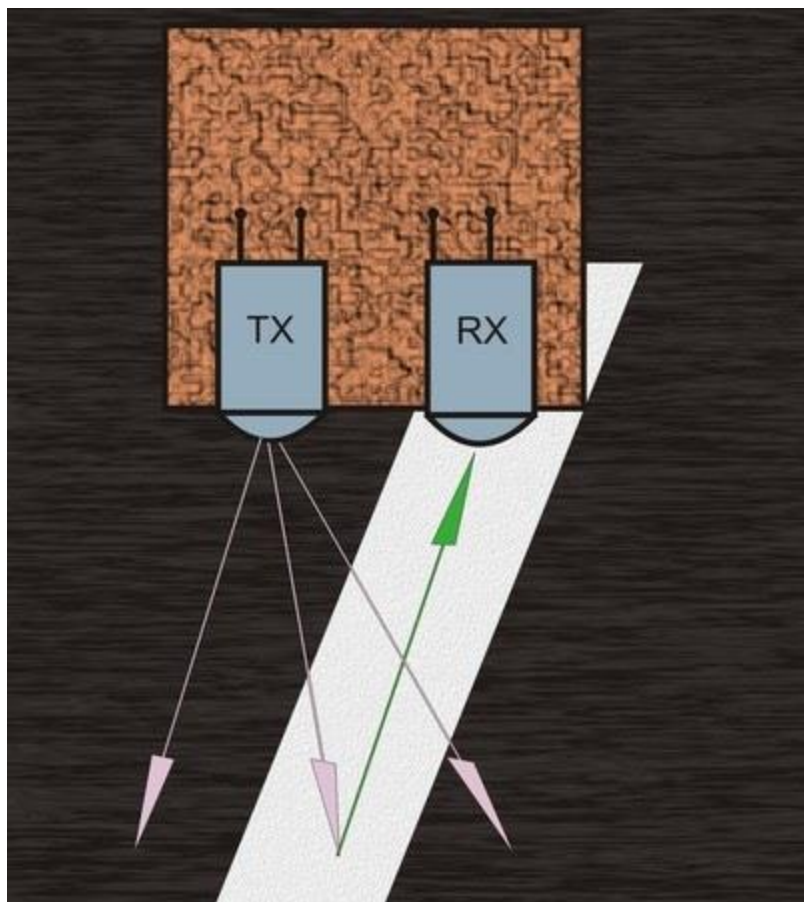


SENSOR OUTPUT

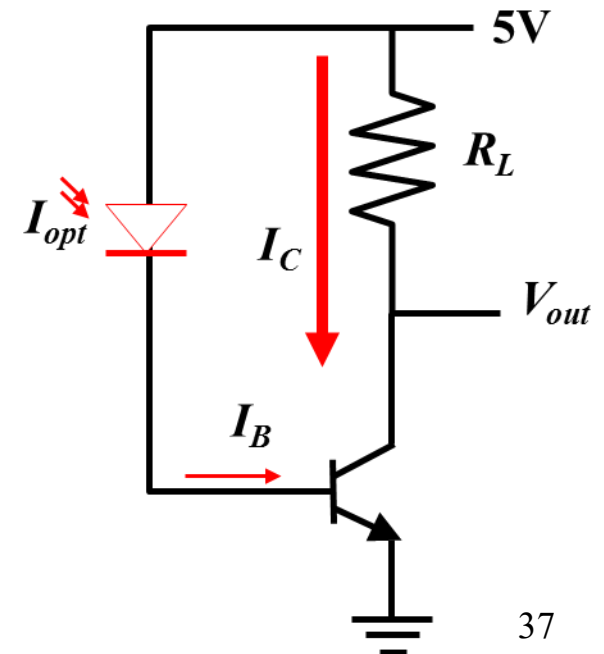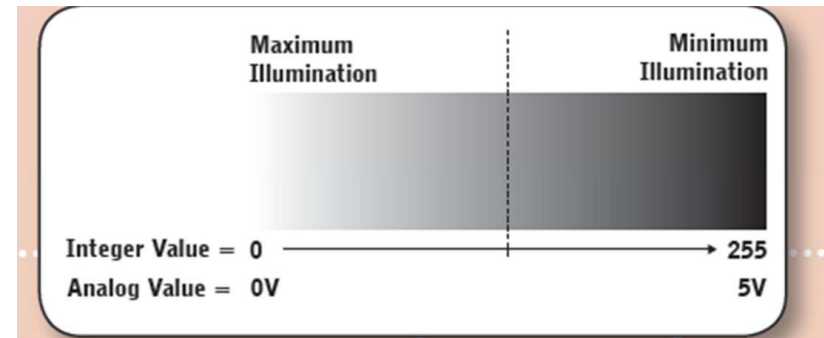- ❖ The sensor output will be around **0 V** when the surface is pale or highly reflective
- ❖ When the reflected light is lower than a certain reference value, the output will be close to 5V
- ❖ By adjusting the reference value, you will be able to distinguish a pale or a dark surface



LINE SENSORS IN YOUR ROBOT

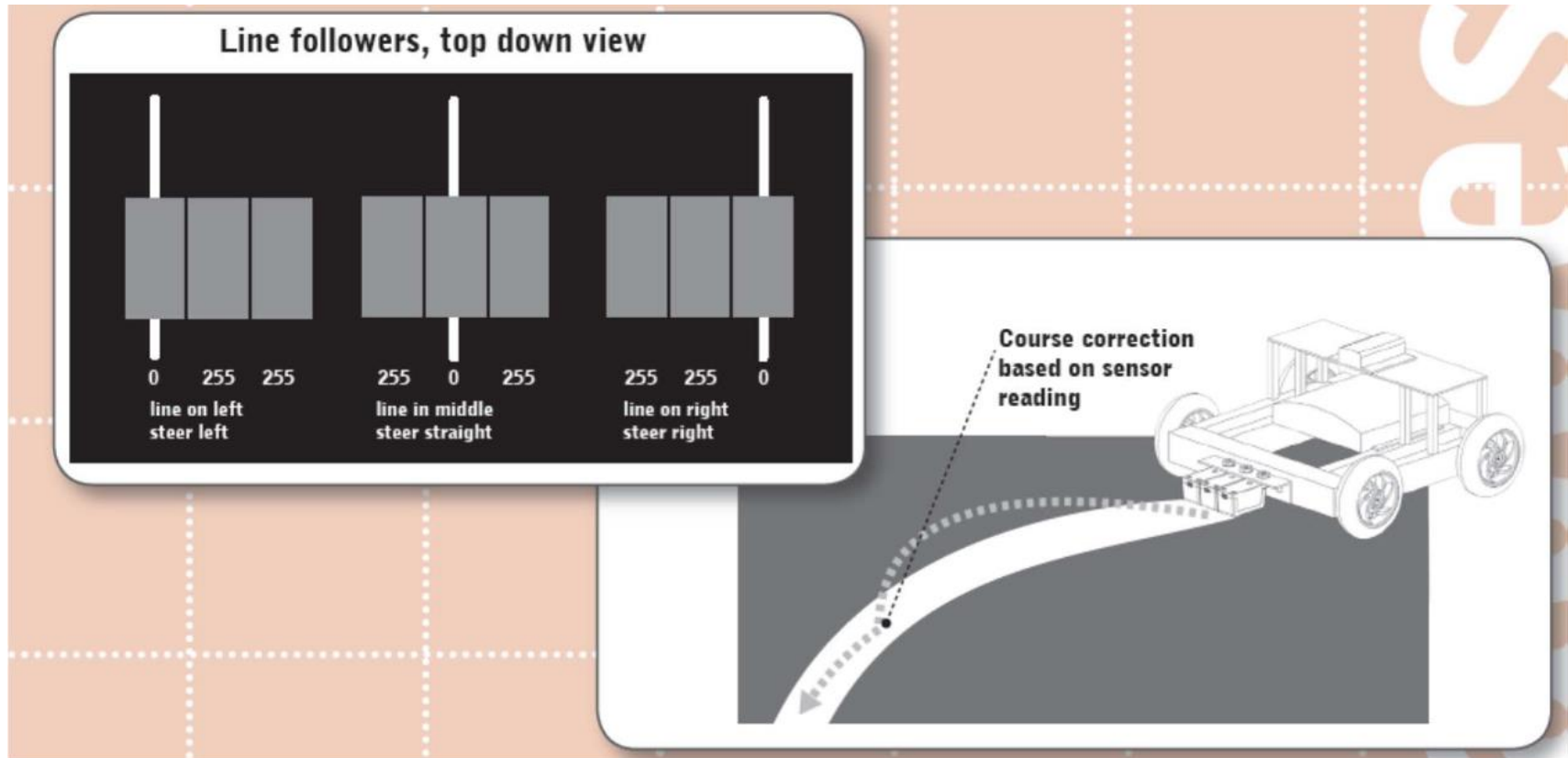
❖ Option 1: Three line sensors are used together



LINE SENSORS IN YOUR ROBOT

❖ Option 2: Two line sensors are used together

<http://www.ermicro.com/blog>

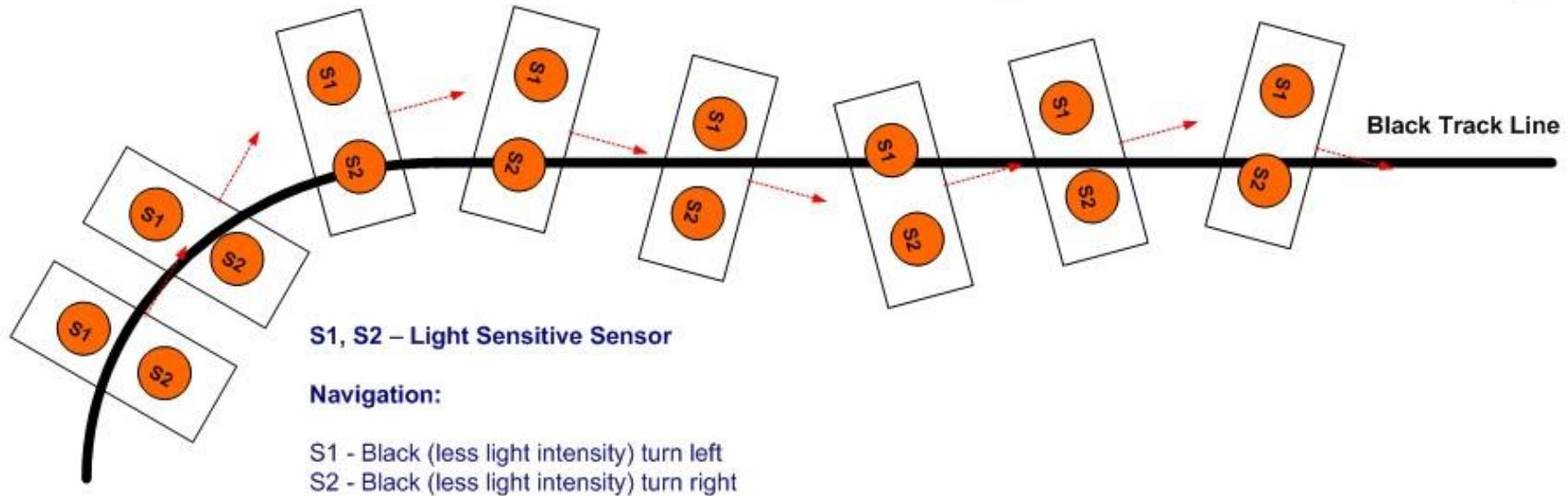

Example of Line tracking navigation on the Line Follower Robot (LFR)



<https://www.youtube.com/watch?v=Cf-V-giXiRw>

ANALOG AND DIGITAL REPRESENTATION OF CURRENT


- ❖ After sensor detects the signal, it has to be represented and stored some where

Analog representation



Stored as voltage or current value

Digital representation

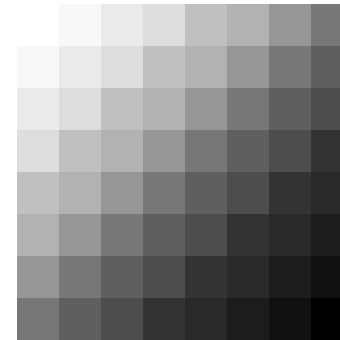


Stored as pulses or numbers

- ❖ Some data loss in digital representation, but more easy to store and duplicate

ANALOG TO DIGITAL CONVERSION

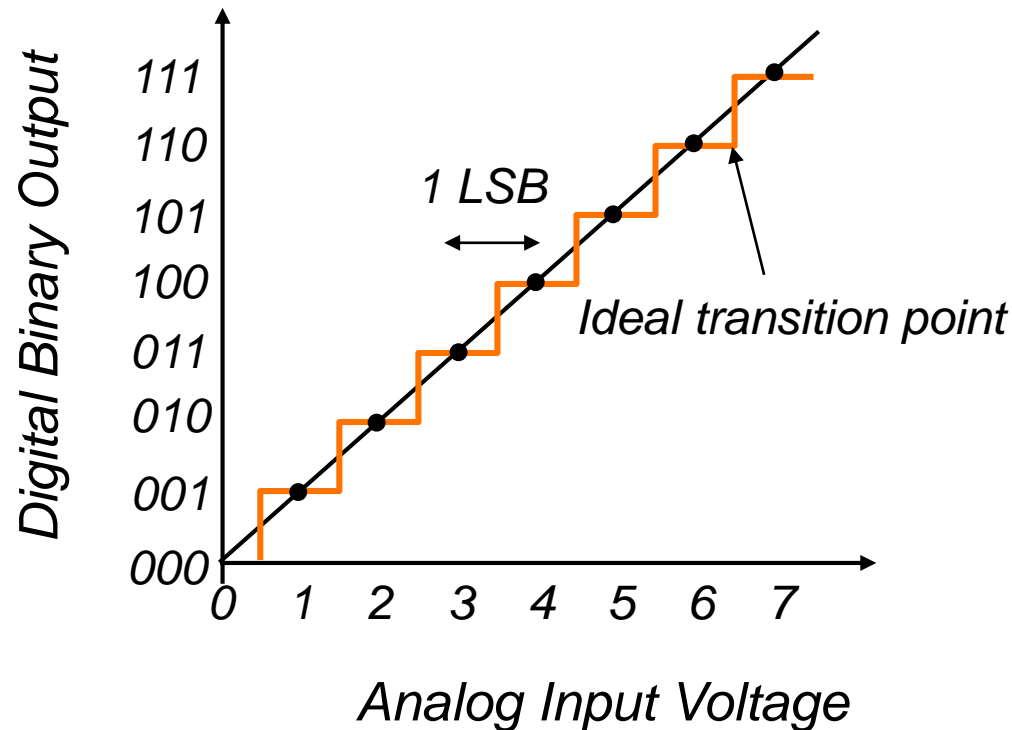❖ Converting a voltage level to binary number and store as 1/0




LSB = Least Significant Bit

$$1 \text{ LSB} = \frac{\text{maximum voltage range}}{\text{number of binary levels}}$$

- The smaller the LSB, the more accurate the conversion and the smaller the quantization error

DATA SAMPLING

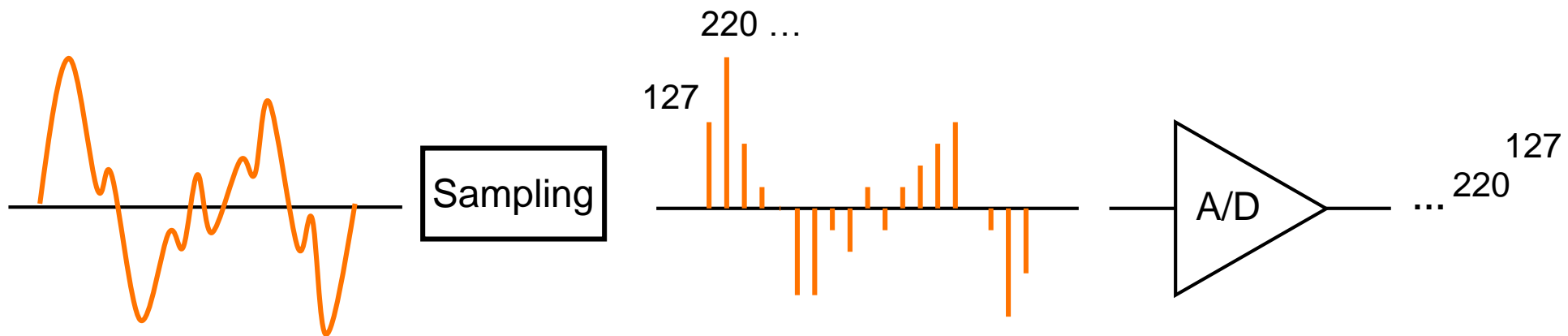
- ❖ Actual A/D process involve sampling, which represents the time domain resolution of the analog signal



- ❖ The more often you sample, the more accurate the data, but the more storage space required
- ❖ For example, CD music is sampled at 44.1kHz









SIGNAL LEVEL AND NOISE

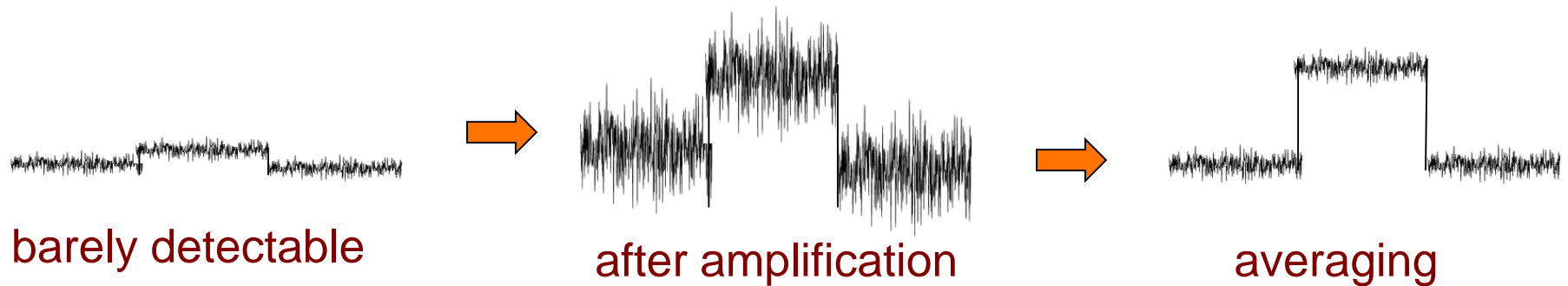- ❖ Signal coming out directly from a sensor is usually very small and need to be amplified
- ❖ All signals contain noise that set the minimum detectable level



- ❖ Most signal from the sensor needs to be amplified
- ❖ For example, your line sensor composed of a sensor and a switch

SUMMARY

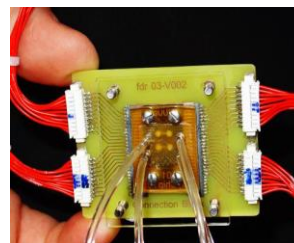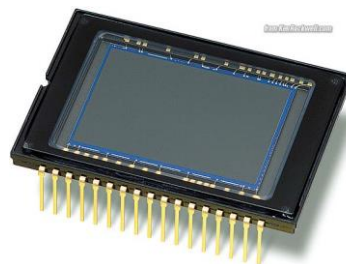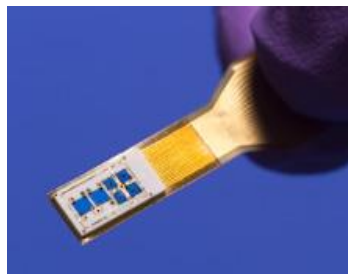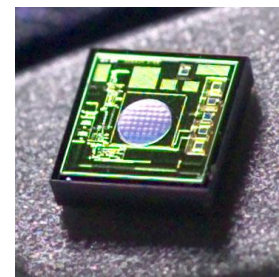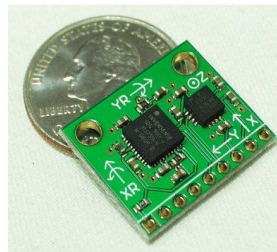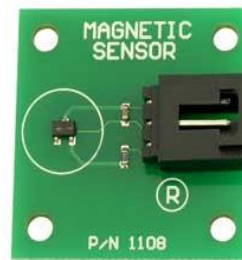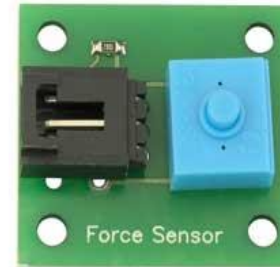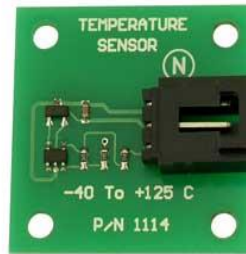

- Sensor signal is usually very small and need to be amplified
- Analog data is converted to digital data through sampling and A/D conversion
- After A/D, sensor data are digitally represented and stored

accelerometer

microphone

chemical sensor

image sensor

biosensor

gyroscope

NEXT LECTURE

- ❖ Logics
- ❖ K-map
- ❖ Midterm Review



Questions ?!