

THE HONG KONG UNIVERSITY OF SCIENCE AND TECHNOLOGY
Department of Electronic and Computer Engineering
ELEC 1100

Laboratory 2: DC Regulation and Pulse Generation (4%)

A) Objectives:

- To construct a regulator to transform DC voltages.
- To generate pulses from a constant supply.

B) Equipment:

- Zener Diode (IN4734), Voltage Regulator (LM7805)
- NE555 Timer, 74HC14 Schmitt Trigger, Resistors, Capacitors

C) Prelab (solution included)

- Q1 What is the difference between a Zener diode and a diode?

Zener diode allows current to flow when reverse voltage is larger than a certain value.


- Q2 For the NE555 IC picture below, circle pin #2. (Hint: Next to big dot is pin 1)
- Q3 In Experiment 3, what should be the frequency and duty cycle of the wave generated?



$$\text{Frequency} = 1/[0.7 \cdot (30k + 2 \cdot 10k) \cdot 0.1\mu] = 286\text{Hz}$$
$$\text{Duty Cycle} = (30k + 10k) / (30k + 2 \cdot 10k) = 0.8$$

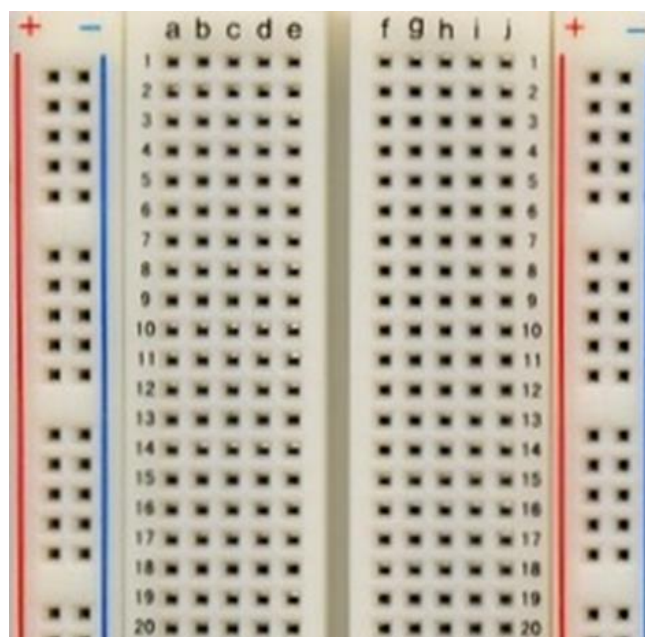- Q4 Draw the breadboard connection of Experiment 2, 3 & 4.


Check with your partner or refer to the tutorial slides



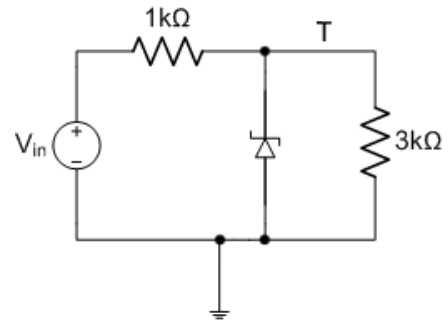D) Experiment Procedures:

Experiment 1: Zener diode regulator (~30 mins)

Step 1: With the new breadboard in your project box, connect the voltage regulator as shown in the figure on the right. The 1N4734 component is the Zener diode. **Note its polarity.**



Step 2: Use the digital multimeter to measure the voltage at joint T *with respect to ground*.

Step 3: Set the power supply (V_{in}) to 0V and turn it on. The multimeter should show 0V.

Step 4: Slowly increase the power supply voltage to 1V. Record the reading of the multimeter.

Step 5: Repeat step 4 by increasing V_{in} with 1V per step until 16V (i.e. 2V, 3V, etc. until 16V).

Q1: Fill in the table in the summary sheet.


Q2: Sketch the result of Q1 on the graph provided in the summary sheet. (T against V_{in})

Q3: According to the graph you got in Q2, what is the breakdown voltage of the Zener diode?


Note: Zener diode circuit is NOT part of your project. You can remove it from the breadboard when you finish Experiment 1.

Experiment 2: LM7805 Voltage Regulator (~30 mins)

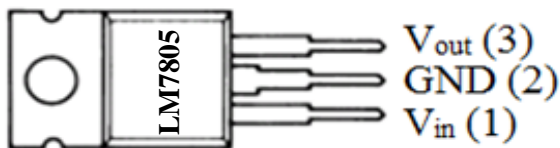Step 1: Take a LM7805 Voltage Regulator. Note its pin diagram shown below.



(the number side is facing up)

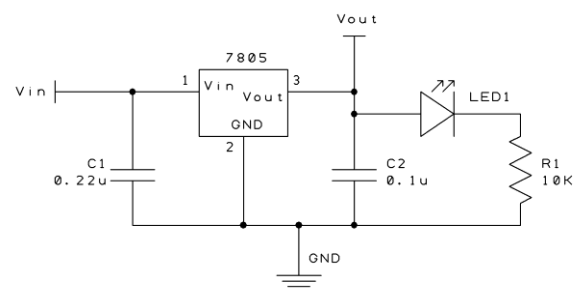

Step 2: Construct the circuit in the figure above (you may refer to the tutorial notes for the breadboard arrangement).

Step 3: Set the power supply to 0V (connect to V_{in}). Connect the digital multimeter to measure the output voltage (V_{out}) *with respect to ground*.

Step 4: Turn on the power supply, slowly increase the voltage to about 8V, the multimeter reading would stay at about 5V. **If it keeps increasing, there is something wrong with the connection. Turn off the power supply. Check your circuit and repeat Step 4.**

Caution: Do NOT touch the regulator LM7805 as its temperature may increase. However, if bad smell comes out, turn off the power supply immediately and ask TAs for help.

Step 5: Increase the input voltage (V_{in}) to 12V and check if the output (V_{out}) is still 5V. Show your TA that you have finished the circuit and obtained 5V output from 12V and get his/her signature.

DO NOT remove the regulator circuit.

Experiment 3: Constructing a pulse generator with NE555 Timer (~30 mins)


Step 1: Take a timer IC (NE555) and construct the circuit shown on the right with the component values below.

$$R_A = 30k\Omega \quad R_B = 10k\Omega \\ C_1 = C_2 = C_3 = 0.1\mu F$$

[The number on the capacitor is read as:

- Digits 1, 2: Significant bits
- Digit 3: Multiplier, i.e. 10^n
- Basic unit: pF ($p = 10^{-12}$)

E.g. "104" = 10×10^4 pF = $0.1\mu F$]

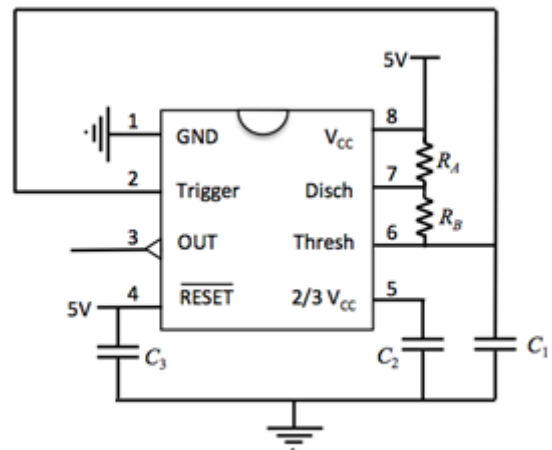

Put this timer circuit below the LM7805 regulator circuit on the breadboard, such that it occupies less space (but keep it tidy), saving space for future labs.

Step 2: Use the 5V from the regulator you obtained in Experiment 2 to be the power supply (you may refer to the tutorial notes for the breadboard arrangement).

Step 3: Measure the voltage on Pin 3 of the IC *with respect to ground* with the oscilloscope.


Q4: Sketch the waveform you see on the DSO (including the scales).

Q5: What is the frequency of the waveform displayed on the screen?


Demo to your TA and obtain his/her signature.

Experiment 4: Pulse generator for your project (~20 mins)

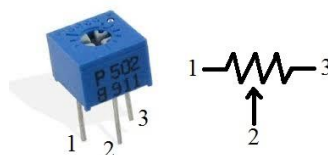Step 1: Take a variable resistor. It looks like this. Note how it connects.



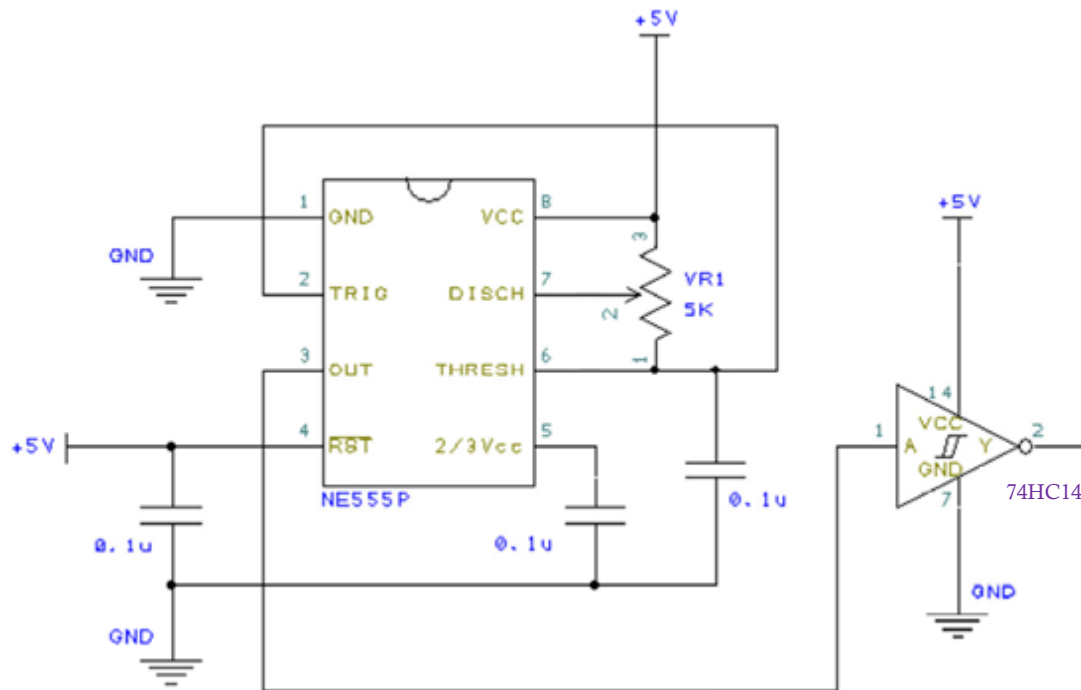Step 2: Replace the resistors R_A and R_B in Experiment 3 with the variable resistor, as shown in the circuit diagram below.



Step 3: Connect a Schmitt Trigger (74HC14) to the output (Pin 3) of the timer.

Step 4: Connect CH1 of the oscilloscope to pin 3 of the timer, and CH2 to pin 2 of the Schmitt Trigger. Press "Auto-Set" to display both waveforms, CH1 at the top and CH2 at the bottom. **Reminder: Set the CRO probes to 1x if necessary.**

Step 5: Using the screwdriver in the project box, adjust the variable resistor until a square wave of frequency 2kHz is obtained. [Demo to your TA and obtain his/her signature.](#)

Q6: Sketch the waveforms you see on the DSO (both CH1 and CH2, including the scales).

Q7: What is the difference between the waveforms in CH1 and CH2?

Keep the circuits you finished on the breadboard for the future.

Remember to clean up your bench! A messy table will cost 3 points!

ELEC 1100 Laboratory 2: Summary Sheet

Group Number: _____

Name: _____ Lab Partner: _____

Student ID:

--	--	--	--	--	--	--	--

Student ID:

--	--	--	--	--	--	--	--


Experimental Part

Experiment 1: Zener diode regulator

Q1: Fill in the table in the answer sheet.

V_{in} (V)	1	2	3	4	5	6	7	8
T (V)								
V_{in} (V)	9	10	11	12	13	14	15	16
T (V)								

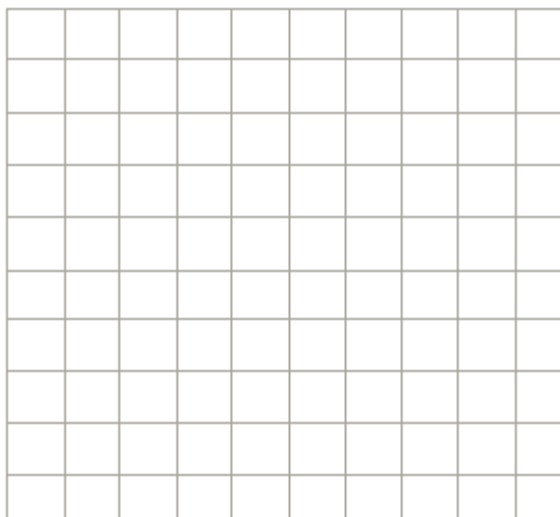Q2: Sketch the result of Q1 on the graph provided. (T against V_{in})



Q3: According to the graph, what is the breakdown voltage of the Zener diode? _____

Experiment 2: LM7805 Voltage Regulator


TA's Signature: _____

Experiment 3: Constructing a pulse generator with NE555 Timer

TA's Signature: _____

Q4: Sketch the waveform you see on the DSO (including the scales).

Q5: What is the frequency of the waveform displayed on the screen?

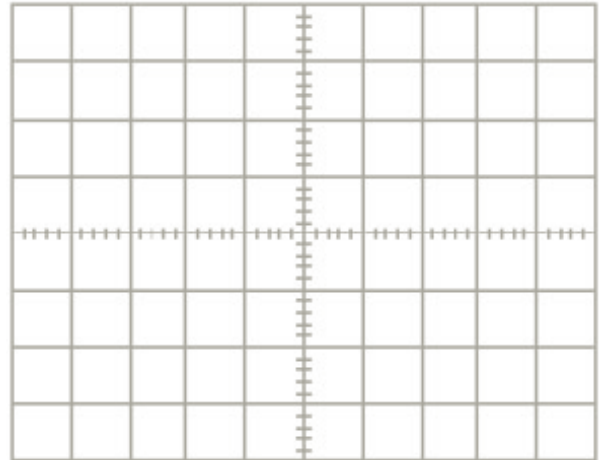

Experiment 4: Pulse generator for your project

TA's Signature: _____

Q6: Sketch the waveforms you see on the DSO (both CH1 and CH2, including the scales).

Q7: What is the difference between the waveforms in CH1 and CH2?

