

Tutorial 5

Assembly of the Navidroid

Power supply



Regulator



12V

5V




Counter

straighten



Schmitt Trigger

clock

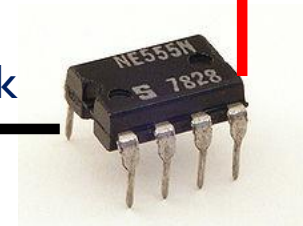


NE555 timer

Comp. Input




Comparator

Dir.

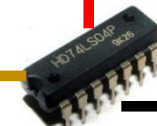

Inverter

PWM signal

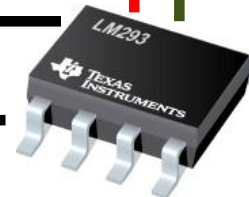


DC Motor Driver




Car

In your lab#05


Lab#2: Regulator

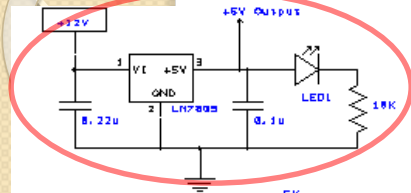


Lab#3: PWM

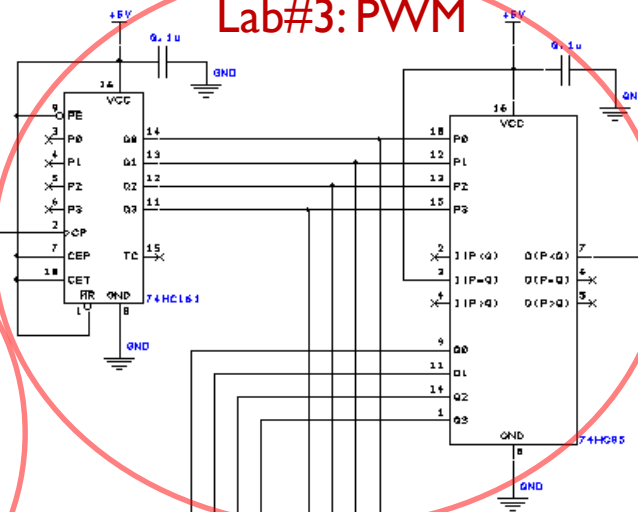


Lab#4: H-bridge

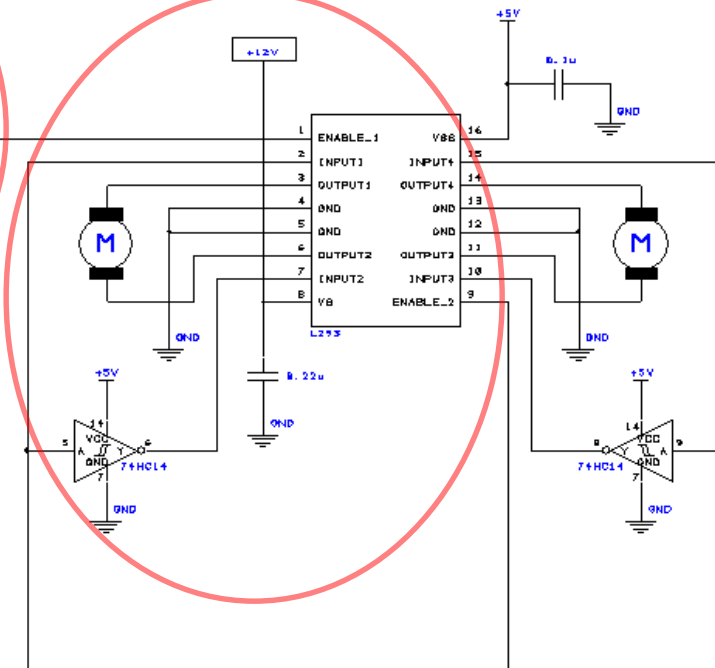



Lab#2: Pulse

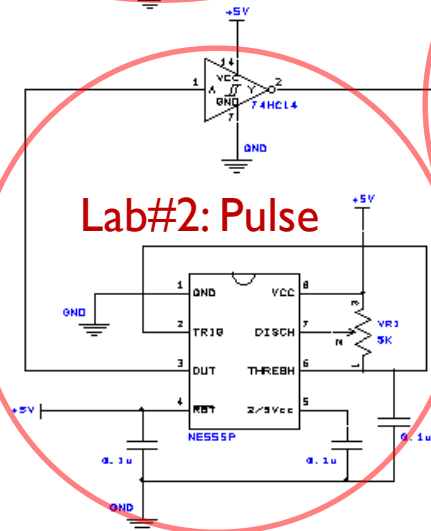

**Your
Logic
Control**

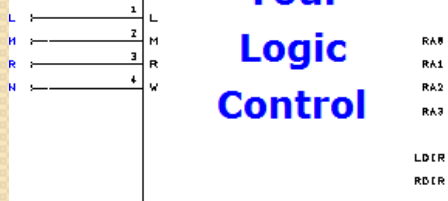


DC Regulator

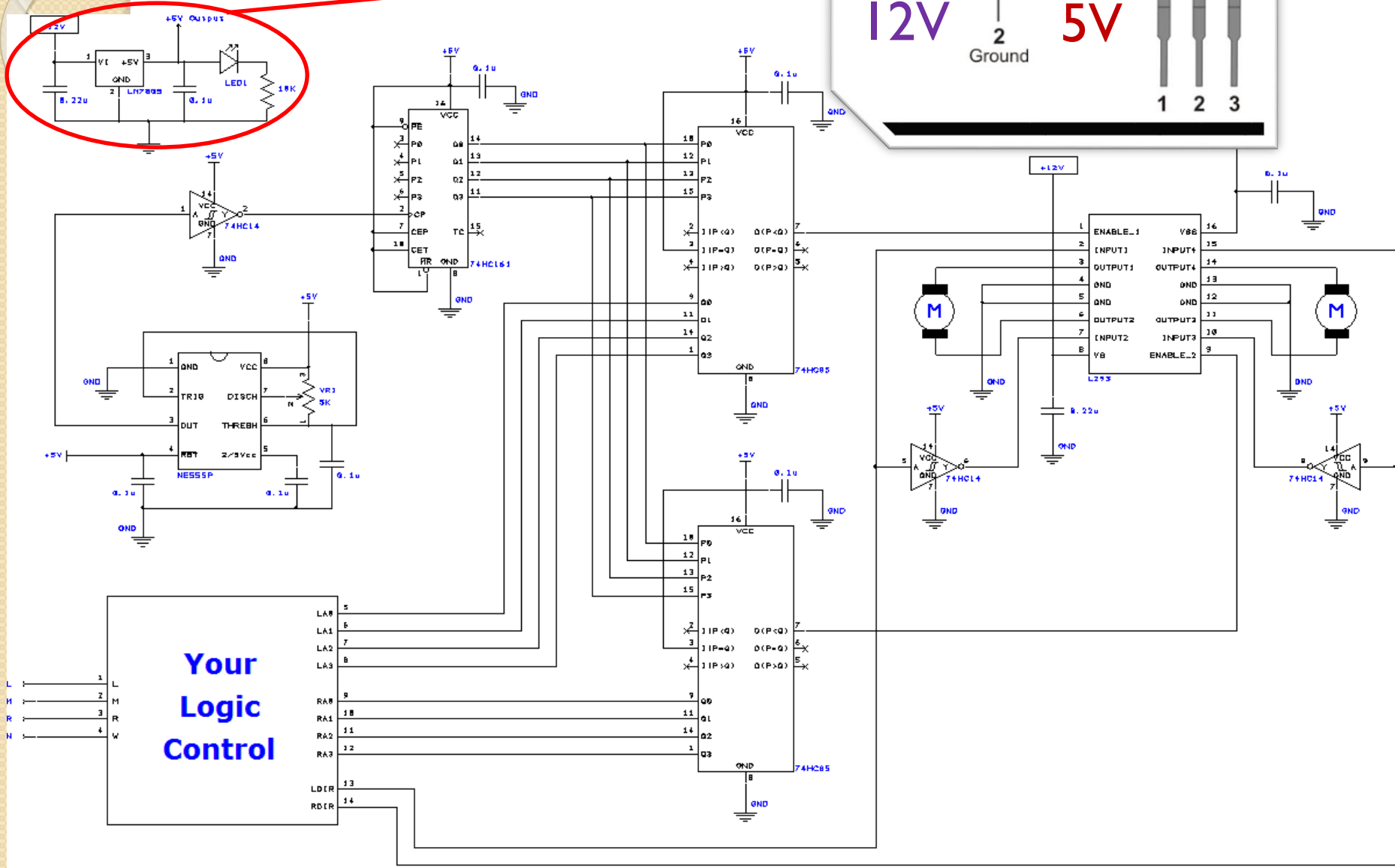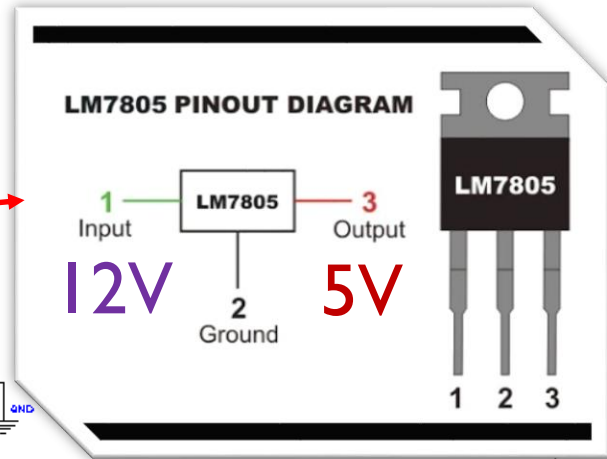

Pulse Generation

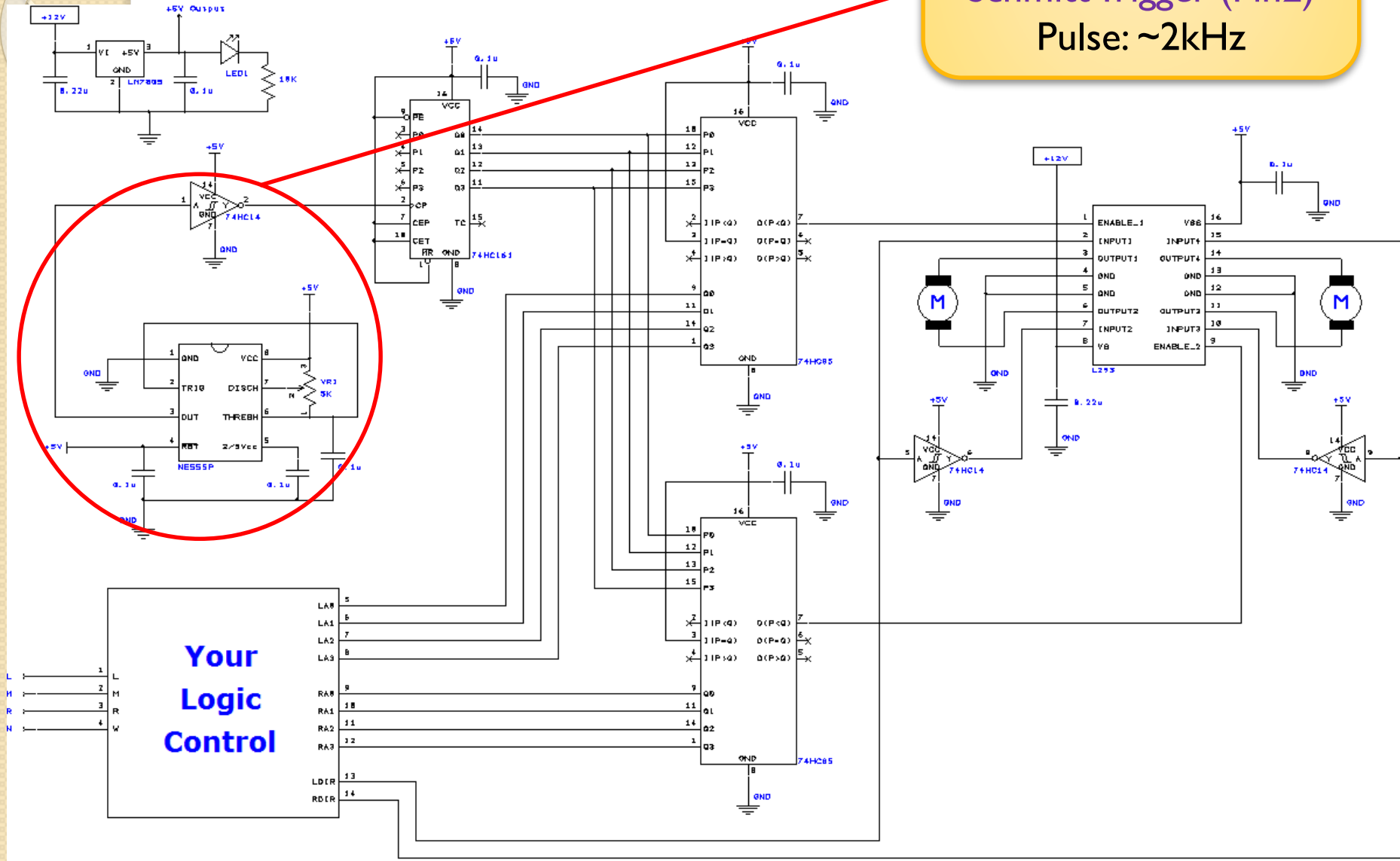
NE555 Timer (Pin3)
+
Schmitt Trigger (Pin2)
Pulse: ~2kHz




PWM Control

Counter (Pins 11-14)
+
Comparator (Pin 7)
PWM: ~125Hz


Lab#3: PWM

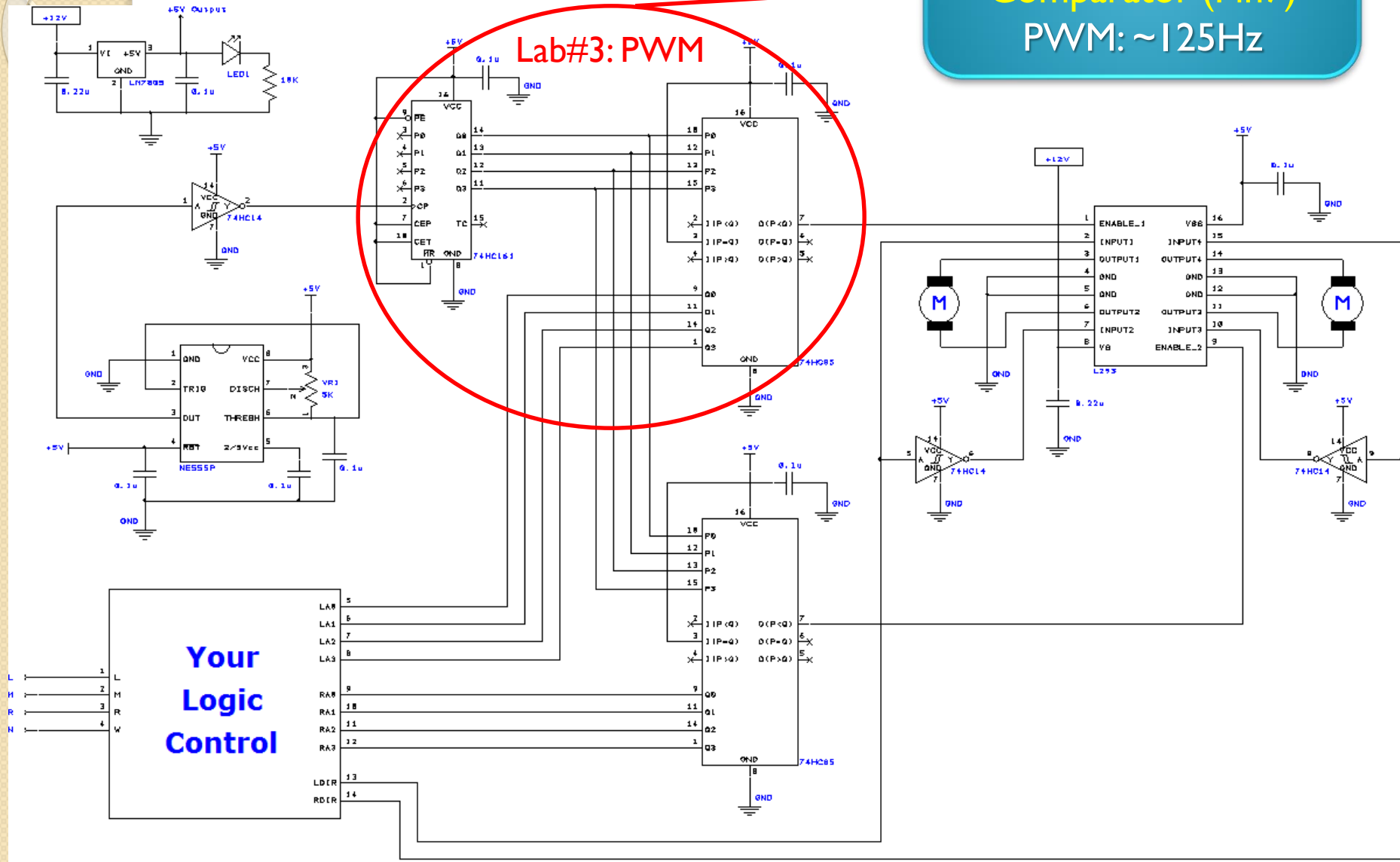


H-bridge Motor Driver

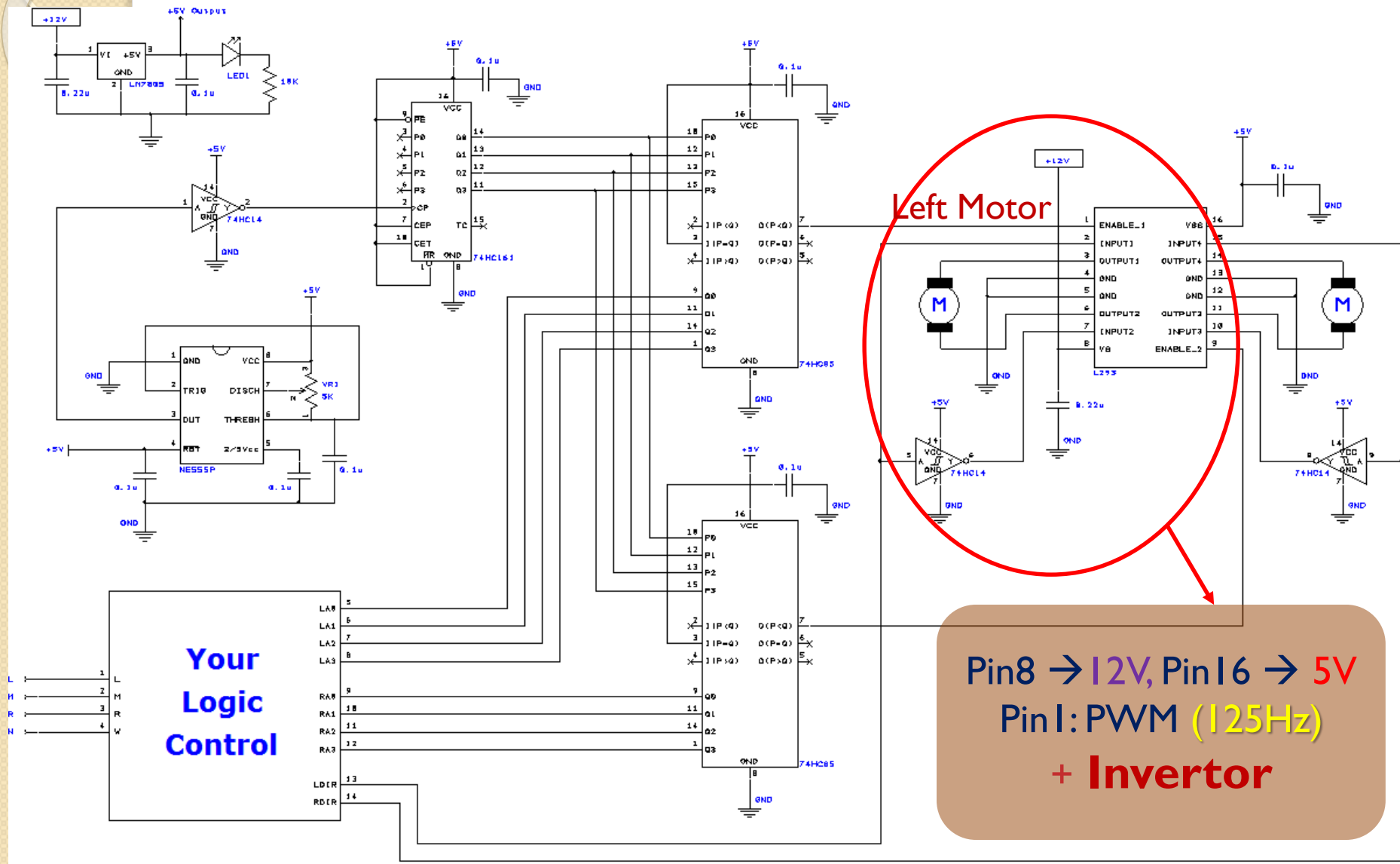

H-bridge Motor Driver

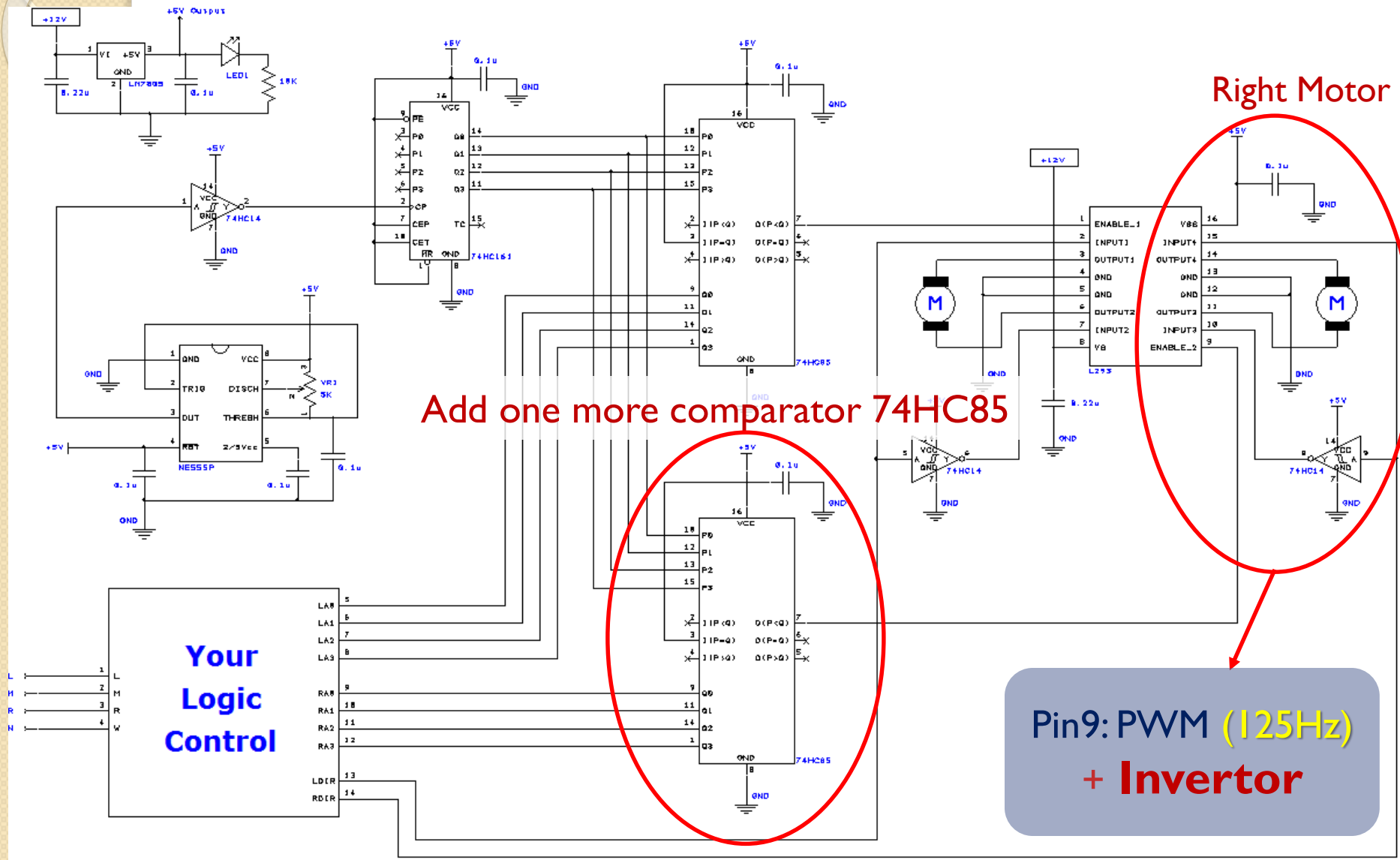

H-bridge Motor Driver

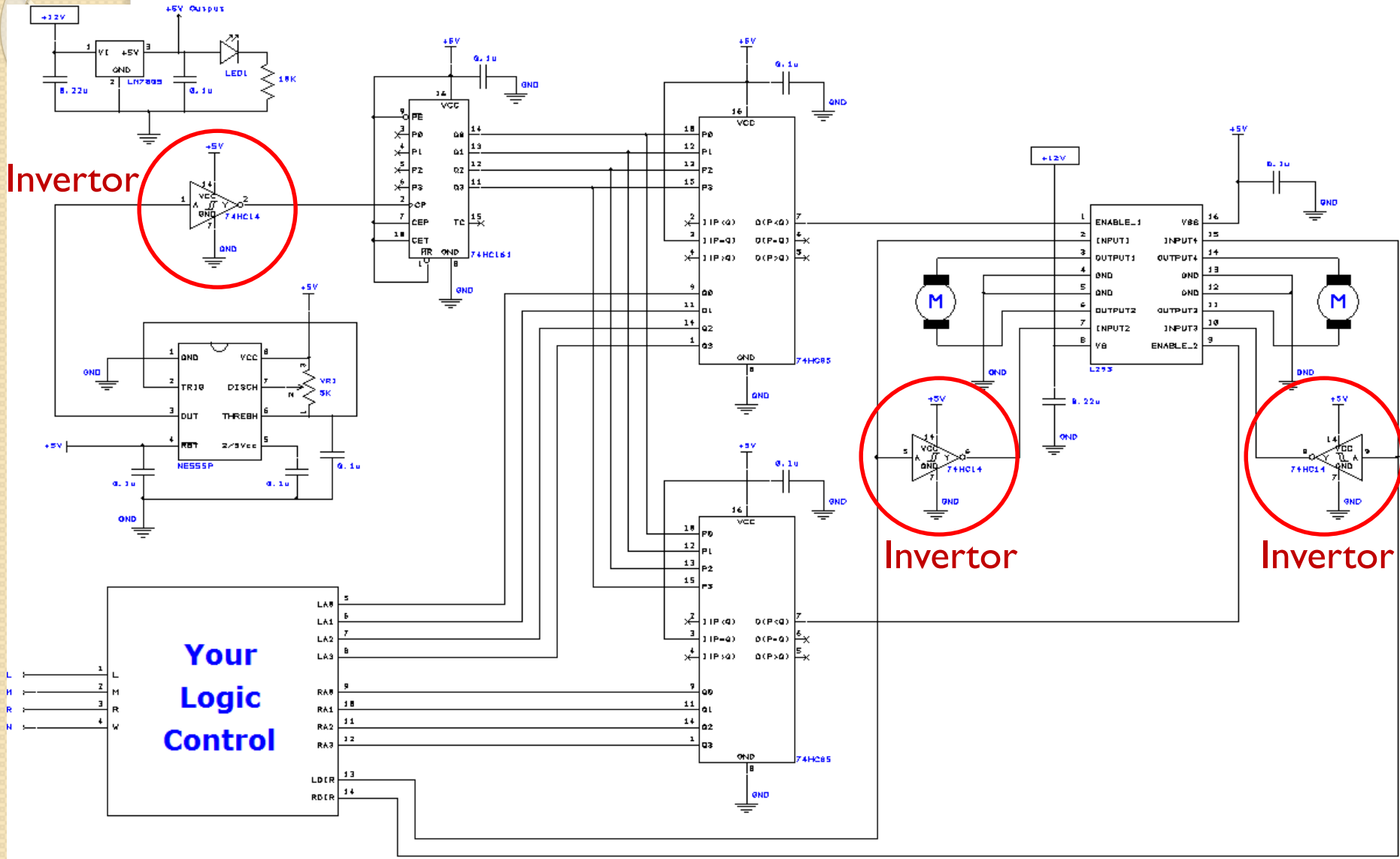


Schmitt Trigger

- The inverter

➤ 6 channels

- Pin 14 → 5V
- Pin 7 → GND

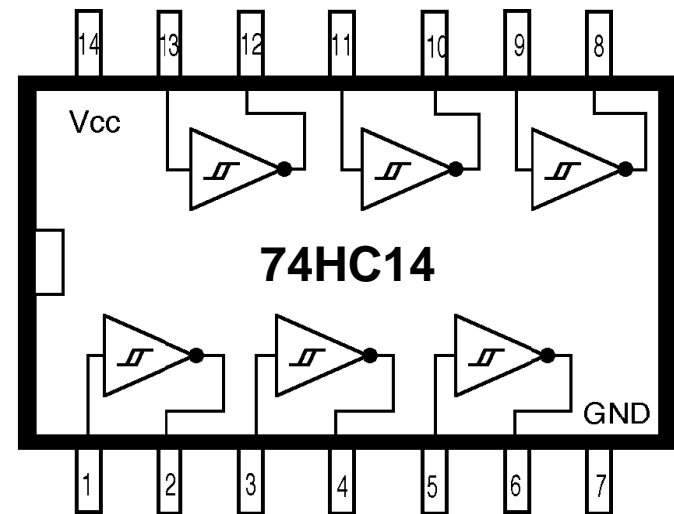

You may use any 3 of them to be the invertors in lab#05

Mini Debugging Report

Describe clearly:

- how you discovered it
- how you found out the source of the bug
- what the bug is
- how you fixed it